

VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of Electric Power Engineering, Electrical Engineering and Electromechanics



THREE-PHASE ELECTRIC CIRCUITS Y CONNECTIONS


by Associate Professor V. Hraniak



OBJECTIVES

- Explain the differences between single-phase, two-phase and three-phase.
- Compute and define the **Balanced Three-Phase** voltages.
- Determine the phase and line voltages/currents for Three-Phase systems.


SINGLE PHASE TWO WIRE

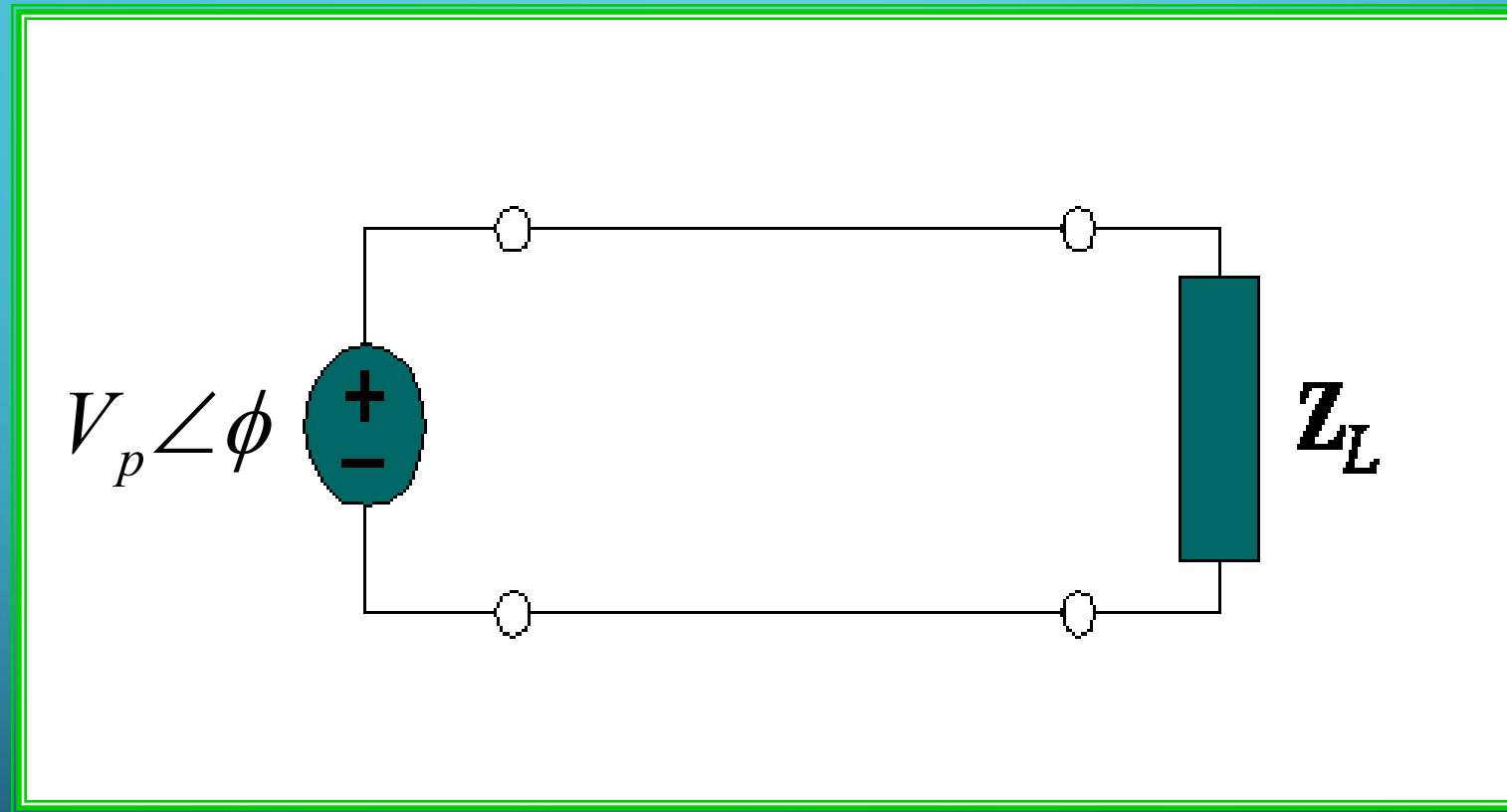

SINGLE PHASE SYSTEM

- A generator connected through a pair of wire to a load – **Single Phase Two Wire.**
- V_p is the magnitude of the source voltage, and ϕ is the phase.

SINLGE PHASE THREE WIRE

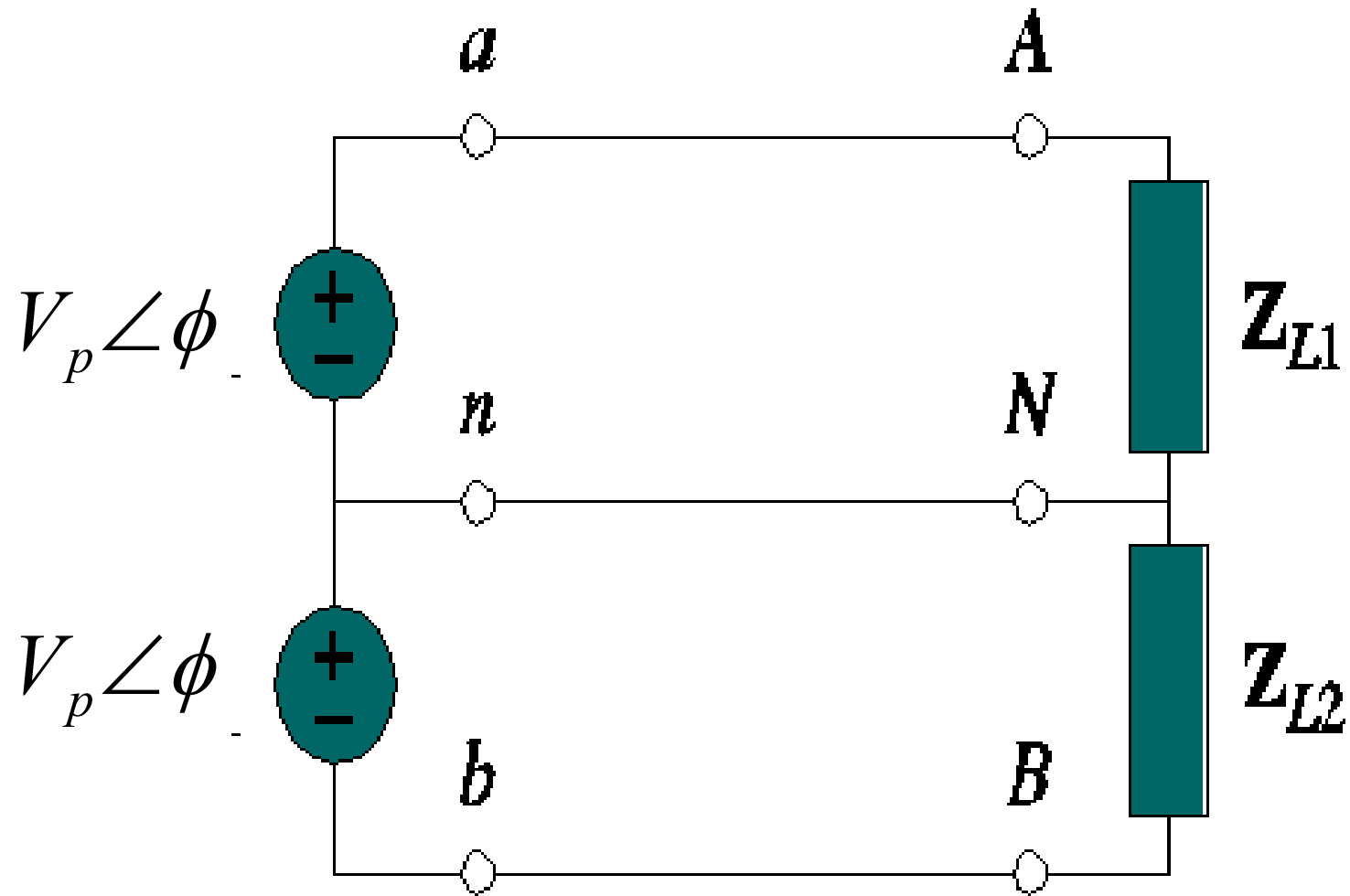


SINGLE PHASE SYSTEM

- Most common in practice: two identical sources connected to two loads by two outer wires and the neutral: **Single Phase Three Wire**.
- Terminal voltages have same magnitude and the same phase.

POLYPHASE SYSTEM

- Circuit or system in which AC sources operate at the same frequency but different phases are known as polyphase.

TWO PHASE SYSTEM THREE WIRE

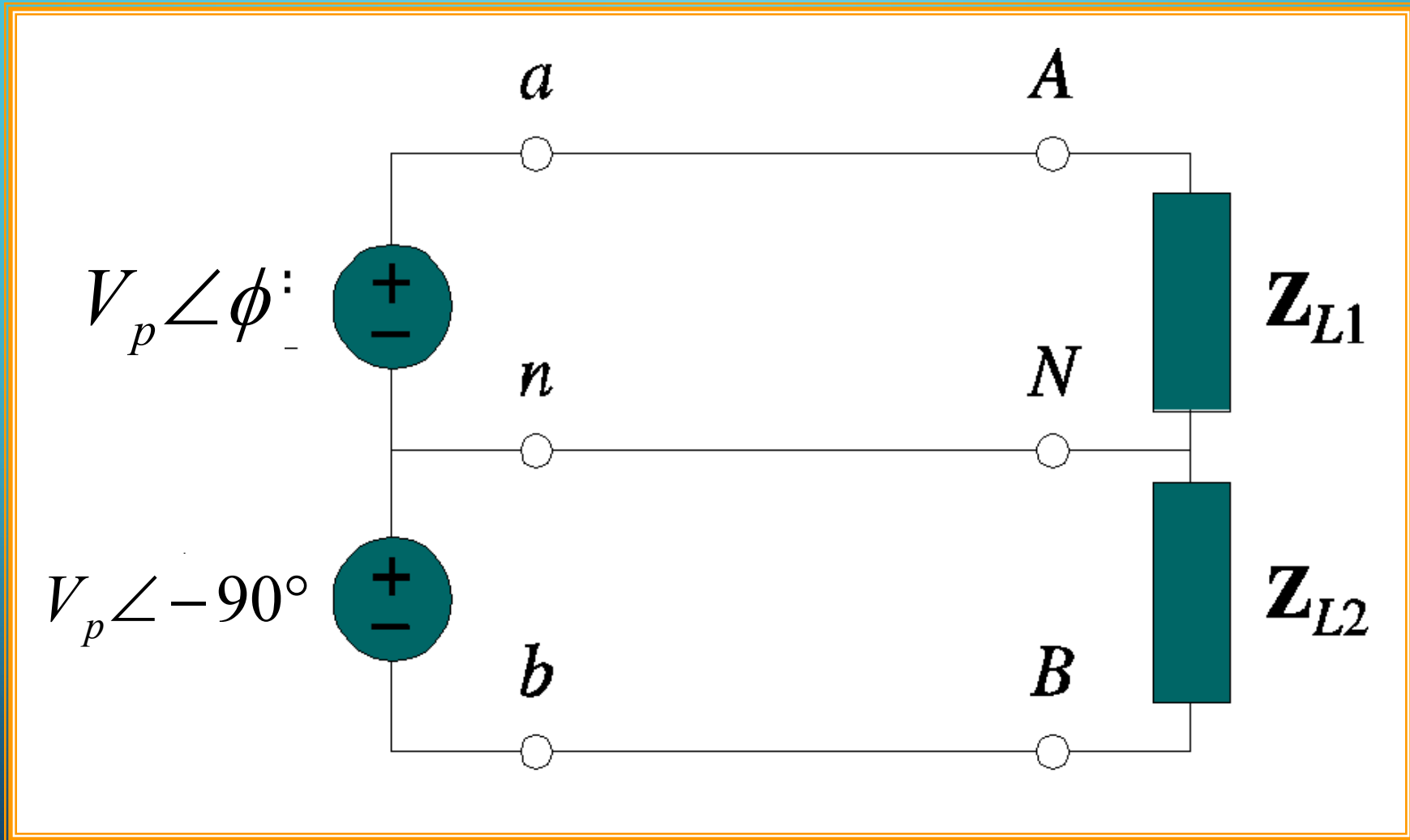


POLYPHASE SYSTEM

- **Two Phase System:**
 - A generator consists of two coils placed perpendicular to each other
 - The voltage generated by one lags the other by 90° .

POLYPHASE SYSTEM

- **Three Phase System:**
 - A generator consists of three coils placed 120° apart.
 - The voltage generated are equal in magnitude but, out of phase by 120° .
- Three phase is the most economical polyphase system.

THREE PHASE FOUR WIRE

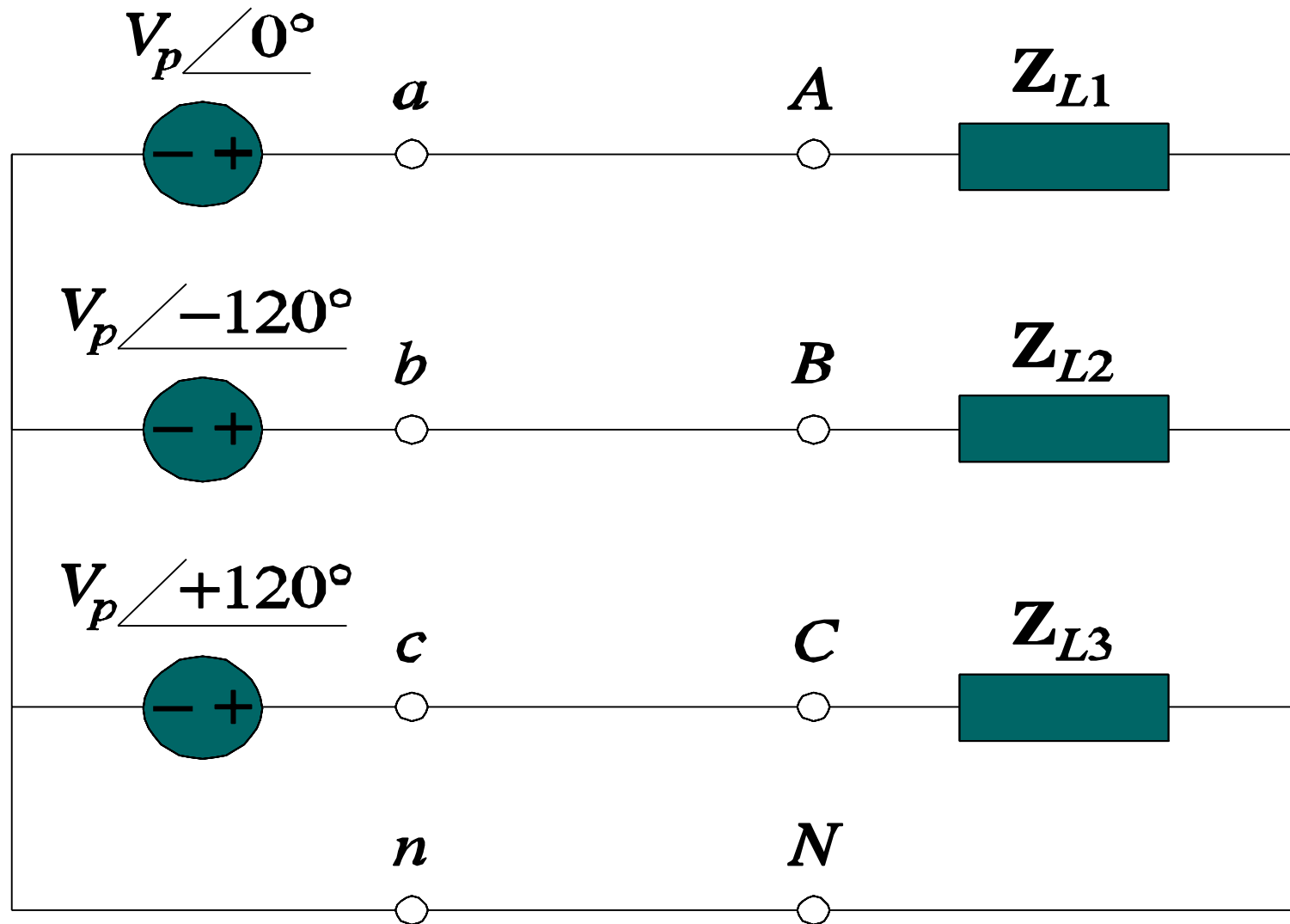

IMPORTANCE OF THREE PHASE SYSTEM

- All electric power is generated and distributed in three phase.
 - One phase, two phase, or more than three phase input can be taken from three phase system rather than generated independently.
 - Melting purposes need 48 phases supply.

IMPORTANCE OF THREE PHASE SYSTEM

- **Uniform power transmission and less vibration of three phase machines.**
 - The instantaneous power in a 3ϕ system can be constant (not pulsating).
 - High power motors prefer a steady torque especially one created by a rotating magnetic field.

IMPORTANCE OF THREE PHASE SYSTEM

- **Three phase system is more economical than the single phase.**
 - The amount of wire required for a three phase system is less than required for an equivalent single phase system.
 - Conductor: Copper, Aluminum, etc




THREE PHASE GENERATION


GENERATOR WORK

- The generator consists of a rotating magnet (**rotor**) surrounded by a stationary winding (**stator**).
- Three separate windings or coils with terminals a-a', b-b', and c-c' are physically placed 120° apart around the stator.

GENERATION OF THREE-PHASE AC

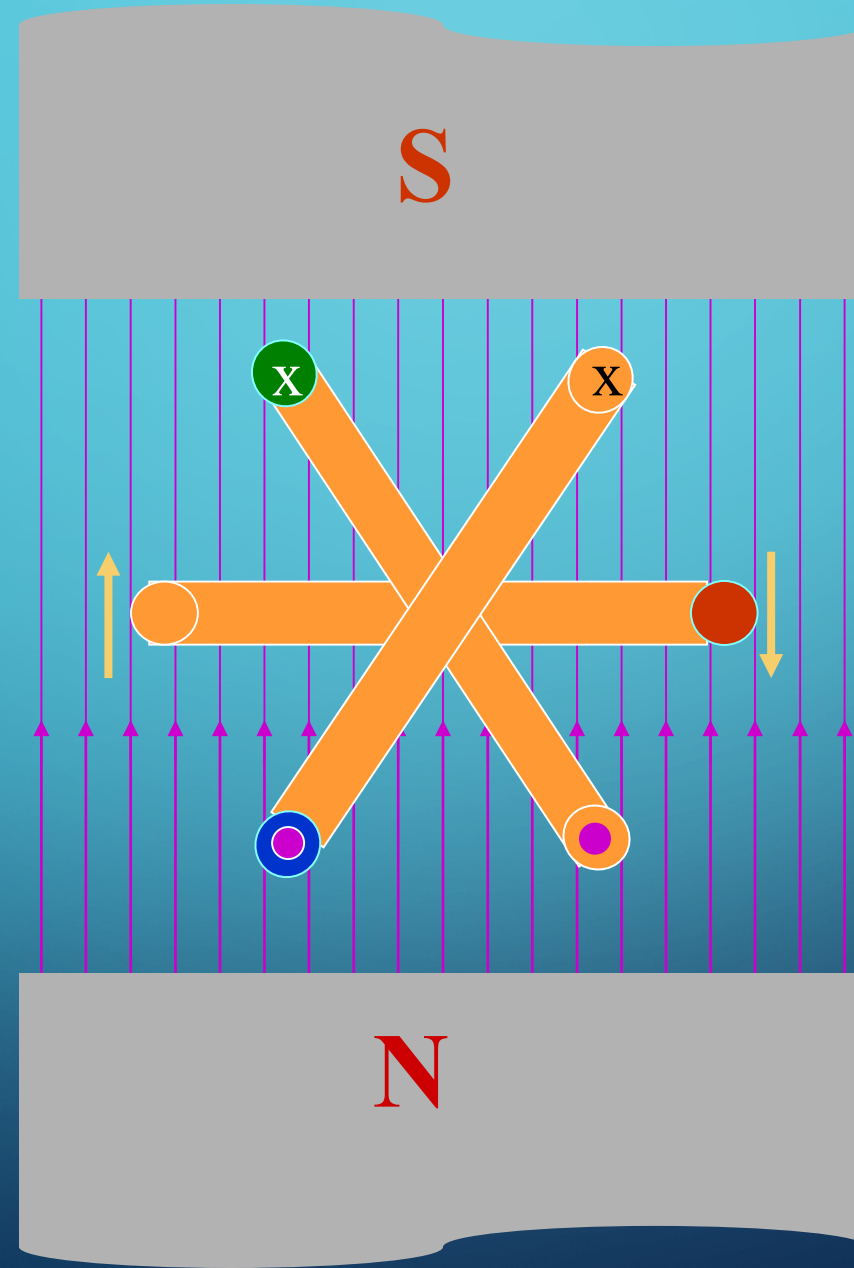

THREE-PHASE WAVEFORM

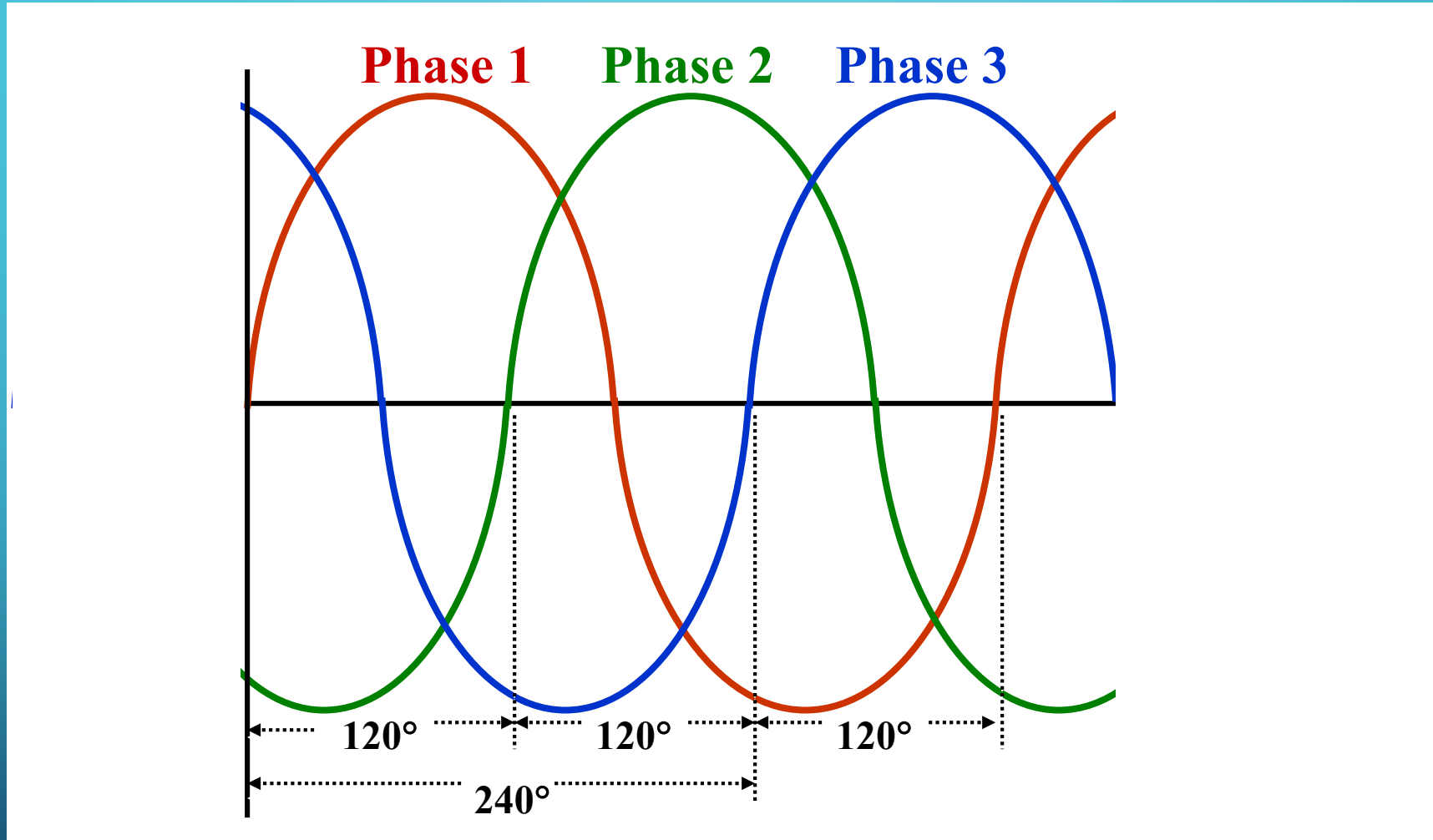


Phase 2 lags **phase 1** by 120°.

Phase 3 lags **phase 1** by 240°.


Phase 2 leads **phase 3** by 120°.

Phase 1 leads **phase 3** by 240°.

GENERATION OF 3 ϕ VOLTAGES

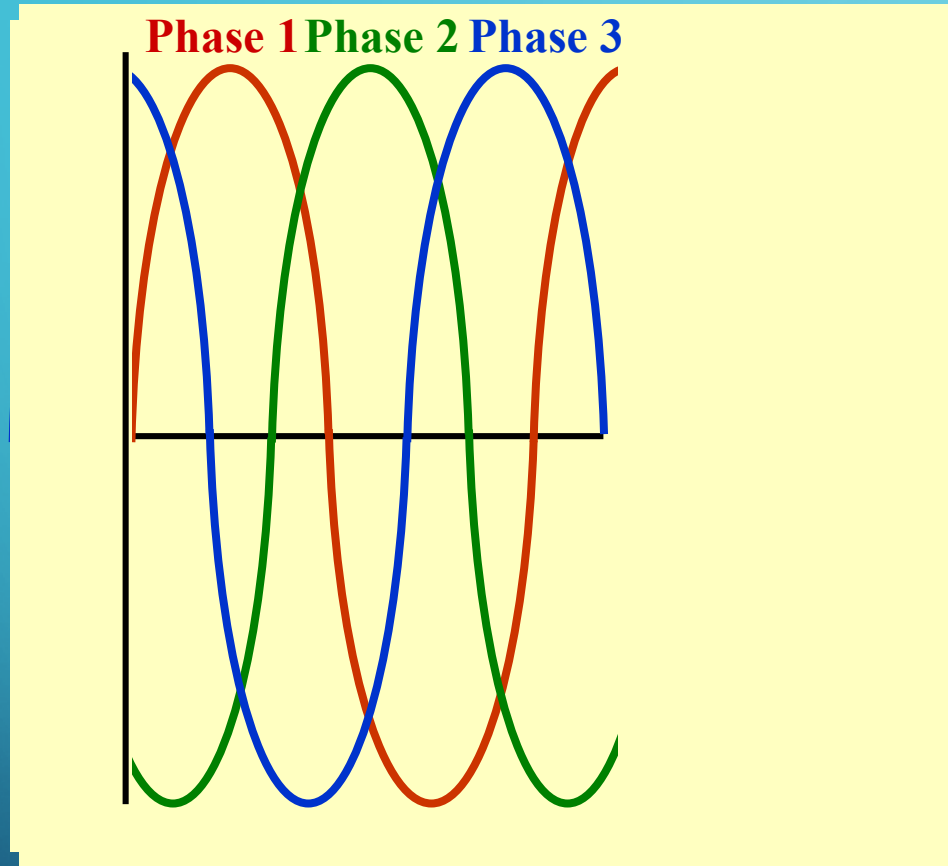

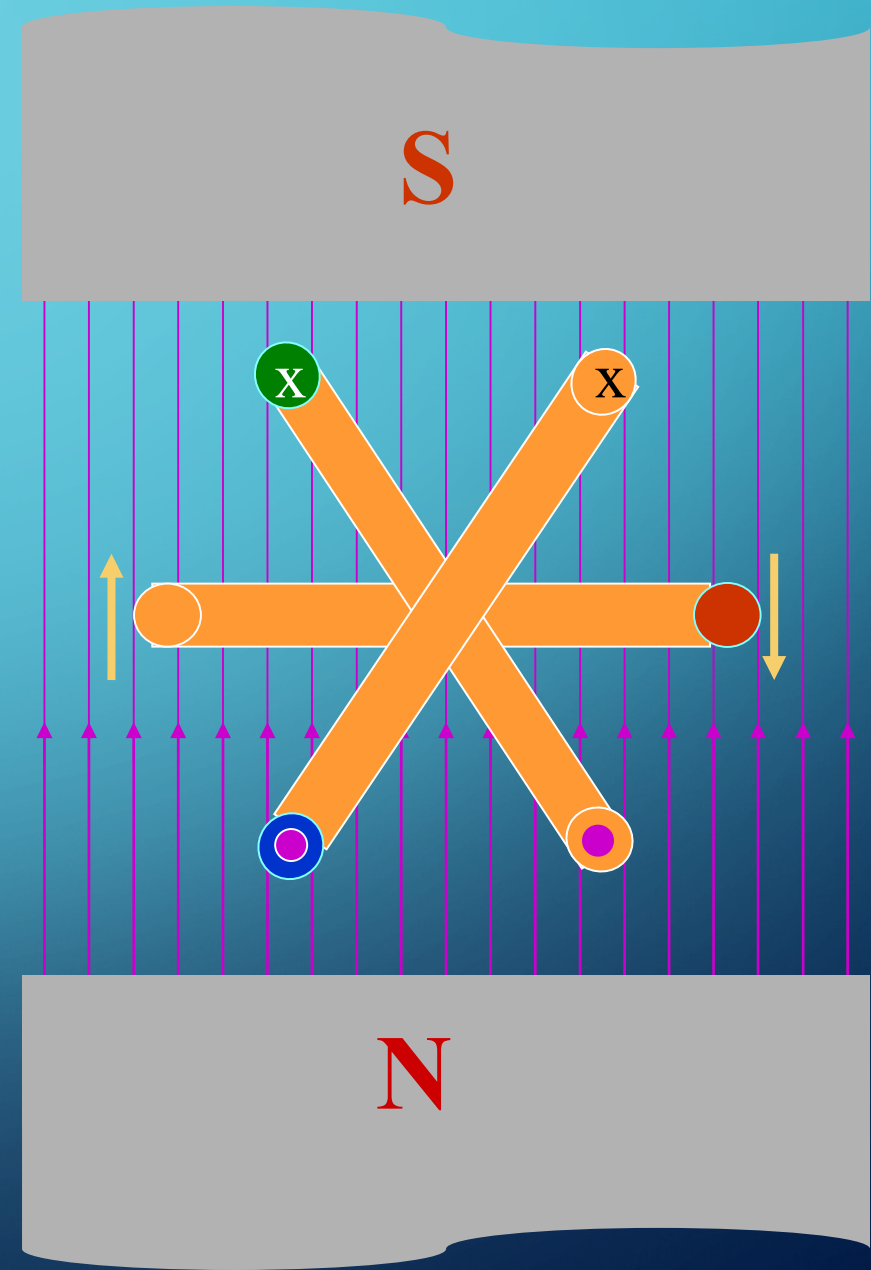Phase 1 is ready to go positive.
Phase 2 is going more negative.
Phase 3 is going less positive.





THREE PHASE QUANTITIES

BALANCED 3 ϕ VOLTAGES

- Balanced three phase voltages:
 - same magnitude (V_M)
 - 120° phase shift

$$v_{an}(t) = V_M \cos(\omega t)$$

$$v_{bn}(t) = V_M \cos(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_M \cos(\omega t - 240^\circ) = V_M \cos(\omega t + 120^\circ)$$

BALANCED 3 ϕ CURRENTS

- Balanced three phase currents:
 - same magnitude (I_M)
 - 120° phase shift

$$i_a(t) = I_M \cos(\omega t - \theta)$$

$$i_b(t) = I_M \cos(\omega t - \theta - 120^\circ)$$

$$i_c(t) = I_M \cos(\omega t - \theta - 240^\circ)$$

PHASE SEQUENCE

$$v_{an}(t) = V_M \cos \omega t$$

$$v_{bn}(t) = V_M \cos(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_M \cos(\omega t + 120^\circ)$$

$$V_{an} = V_M \angle 0^\circ$$

$$V_{bn} = V_M \angle -120^\circ$$

$$V_{cn} = V_M \angle +120^\circ$$

**POSITIVE
SEQUENCE**



$$V_{an} = V_M \angle 0^\circ$$

$$V_{bn} = V_M \angle +120^\circ$$

$$V_{cn} = V_M \angle -120^\circ$$

**NEGATIVE
SEQUENCE**

SEQUENCE

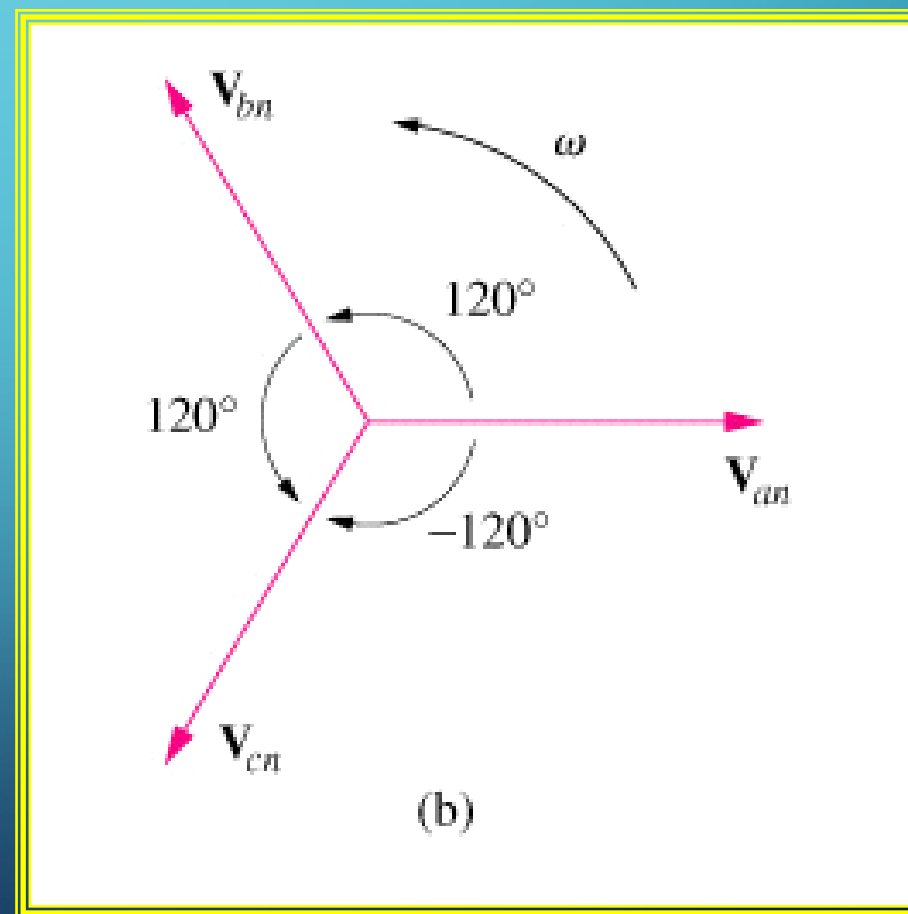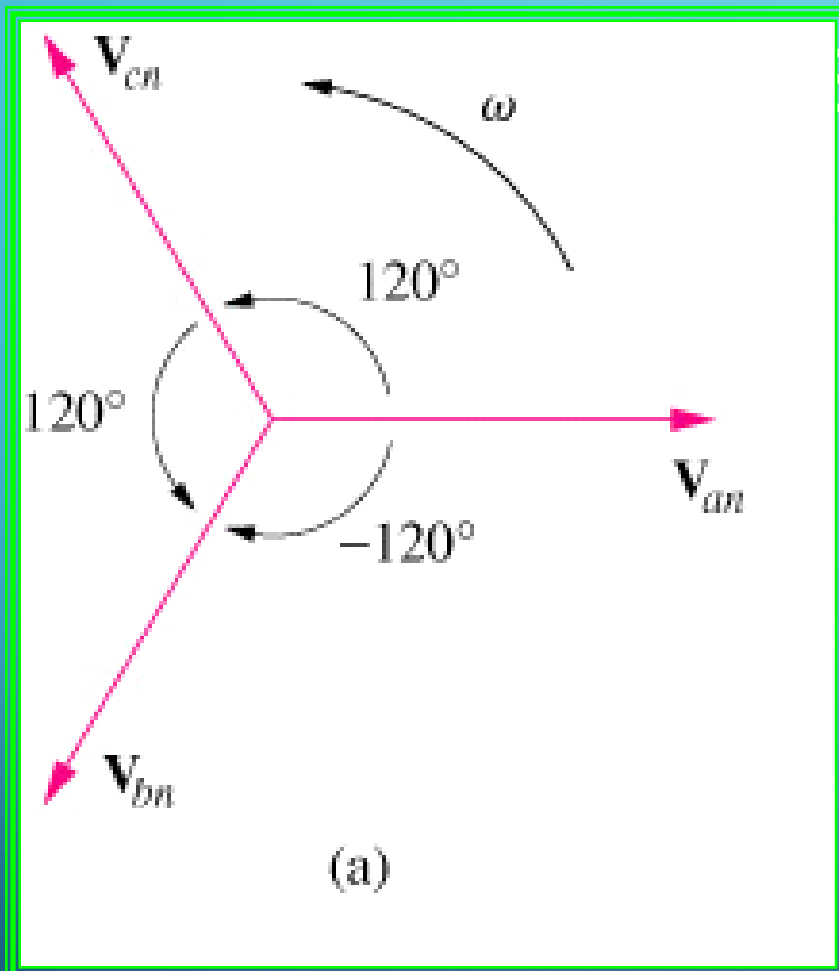

EXAMPLE # 1

- Determine the phase sequence of the set voltages:

$$v_{an} = 200 \cos(\omega t + 10^\circ)$$

$$v_{bn} = 200 \cos(\omega t - 230^\circ)$$

$$v_{cn} = 200 \cos(\omega t - 110^\circ)$$

BALANCED VOLTAGE AND LOAD

- **Balanced Phase Voltage:** all phase voltages are equal in magnitude and are out of phase with each other by 120° .
- **Balanced Load:** the phase impedances are equal in magnitude and in phase.

THREE PHASE CIRCUIT

- POWER
 - The instantaneous power is constant

$$\begin{aligned} p(t) &= p_a(t) + p_b(t) + p_c(t) \\ &= 3 \frac{V_M I_M}{2} \cos(\theta) \\ &= 3 V_{rms} I_{rms} \cos(\theta) \end{aligned}$$

THREE PHASE CIRCUIT

- Three Phase Power,

$$\mathbf{S}_T = \mathbf{S}_A + \mathbf{S}_B + \mathbf{S}_C = 3 \mathbf{S}_\phi$$

THREE PHASE QUANTITIES

QUANTITY	SYMBOL
Phase current	I_{ϕ}
Line current	I_L
Phase voltage	V_{ϕ}
Line voltage	V_L

PHASE VOLTAGES AND LINE VOLTAGES

- **Phase voltage** is measured between the neutral and any line: line to neutral voltage
- **Line voltage** is measured between any two of the three lines: line to line voltage.

PHASE CURRENTS AND LINE CURRENTS

- Line current (I_L) is the current in each **line** of the source or load.
- Phase current (I_ϕ) is the current in each **phase** of the source or load.



THREE PHASE CONNECTION

SOURCE-LOAD CONNECTION

SOURCE	LOAD	CONNECTION
Wye	Wye	Y-Y
Wye	Delta	Y- Δ
Delta	Delta	Δ - Δ
Delta	Wye	Δ -Y


SOURCE-LOAD CONNECTION

- **Common connection of source: WYE**
 - Delta connected sources: the circulating current may result in the delta mesh if the three phase voltages are slightly unbalanced.
- **Common connection of load: DELTA**
 - Wye connected load: neutral line may not be accessible, load can not be added or removed easily.




WYE CONNECTION


WYE CONNECTED GENERATOR

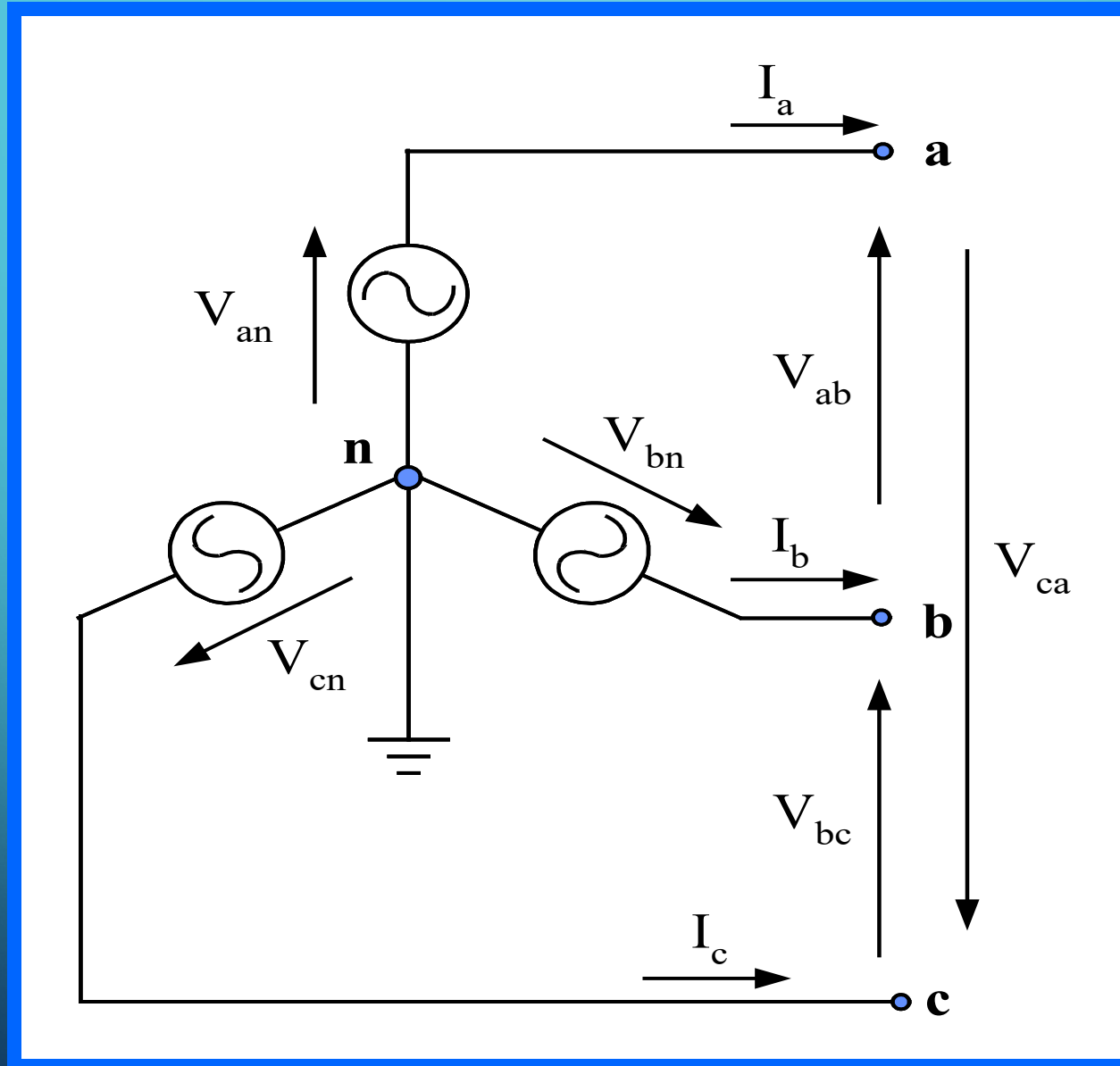


WYE CONNECTED LOAD

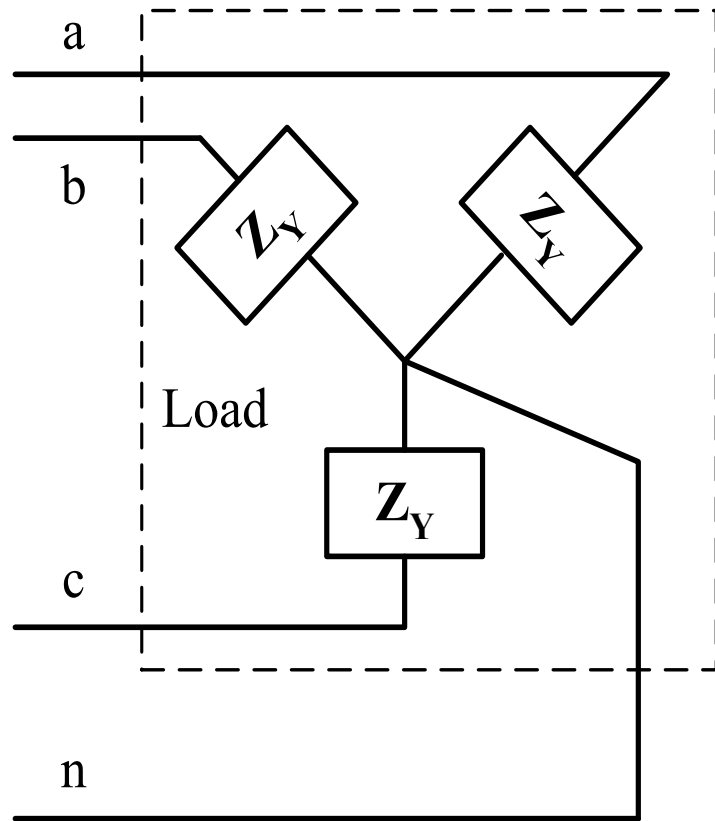

OR

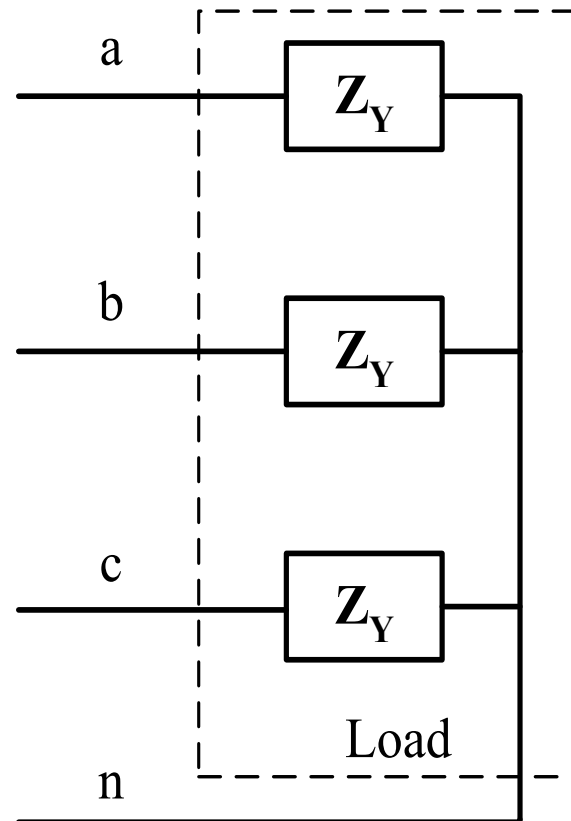

BALANCED Y-Y CONNECTION

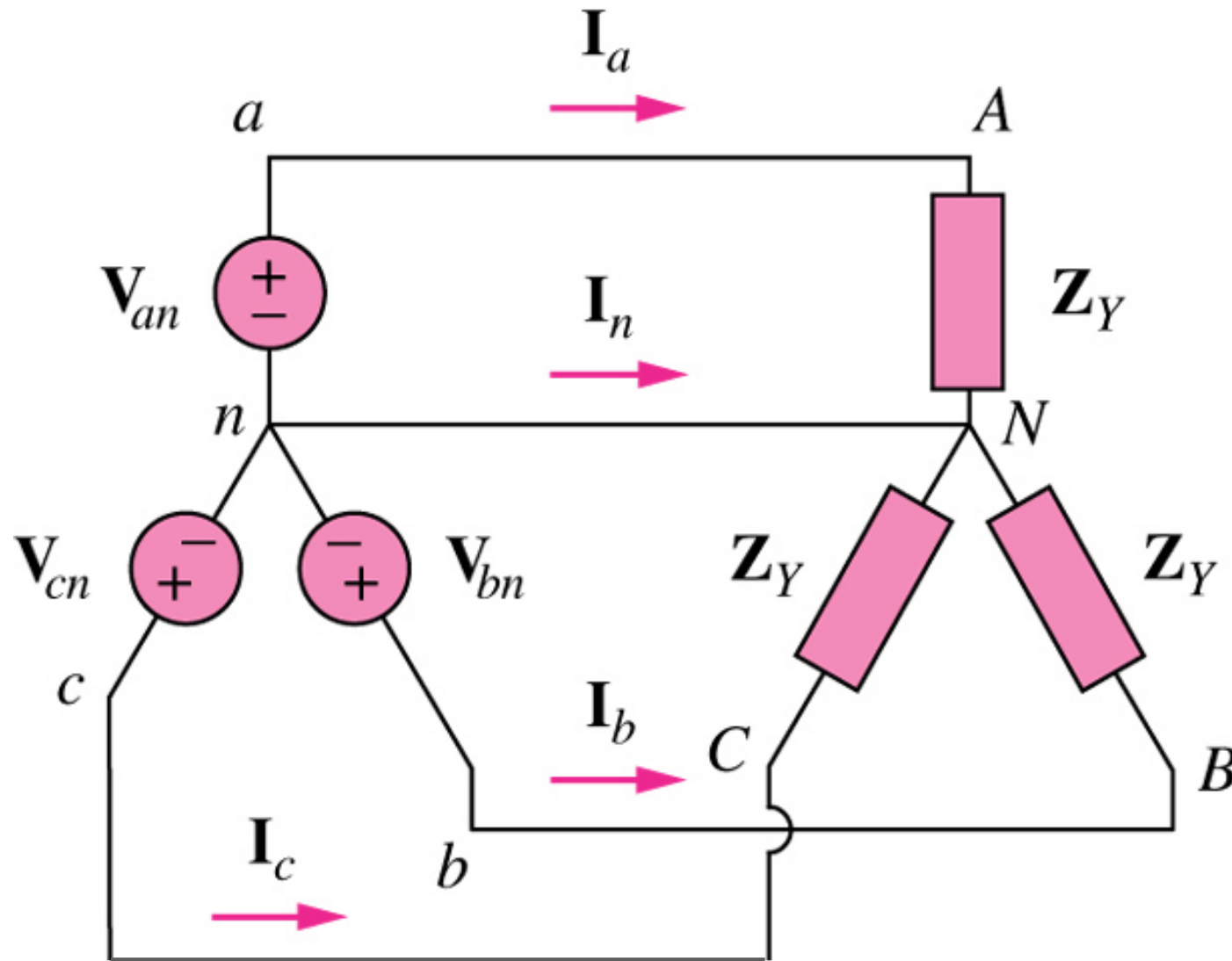


PHASE CURRENTS AND LINE CURRENTS

- In Y-Y system:

$$\mathbf{I}_L = \mathbf{I}_\phi$$

PHASE VOLTAGES, V_ϕ

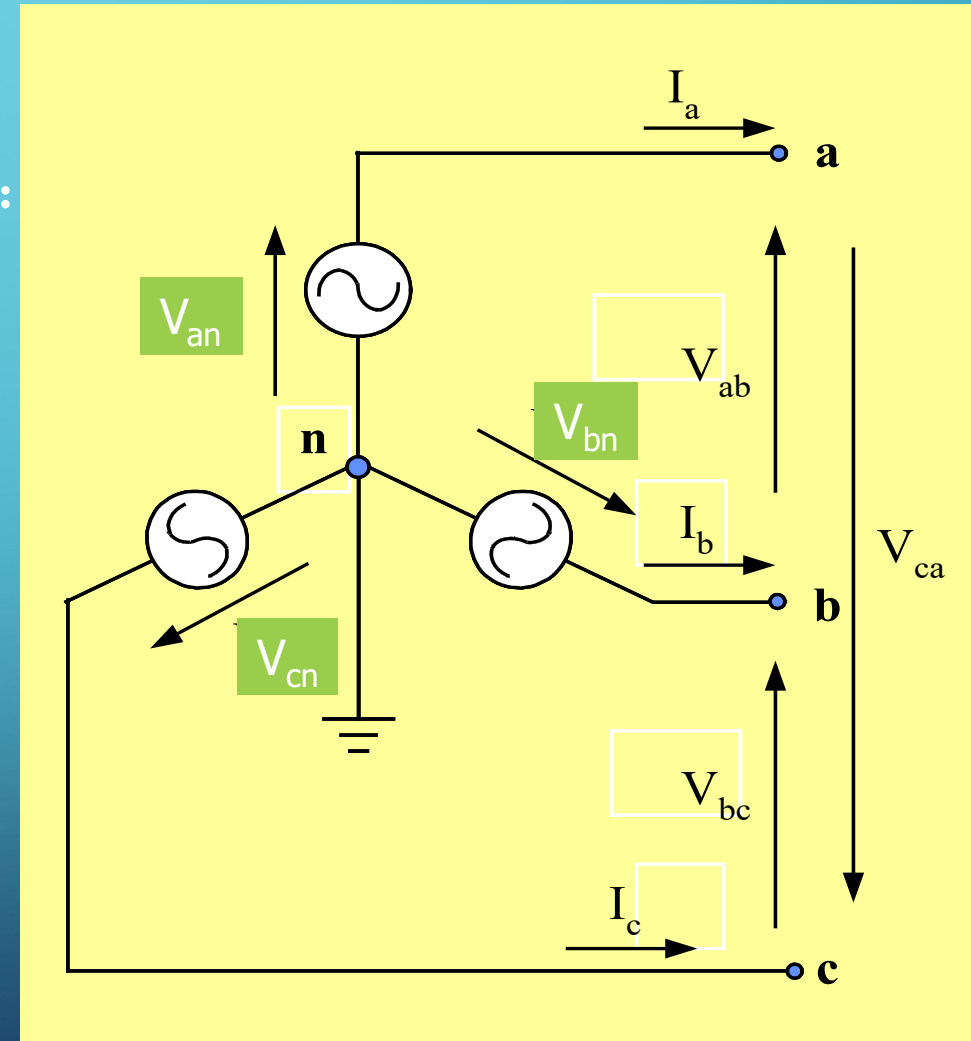- Phase voltage is measured between the neutral and any line: line to neutral voltage



PHASE VOLTAGES, V_{ϕ}


$$V_{an} = V_M \angle 0^{\circ} \quad \text{volt}$$

$$V_{bn} = V_M \angle -120^{\circ} \quad \text{volt}$$

$$V_{cn} = V_M \angle 120^{\circ} \quad \text{volt}$$

LINE VOLTAGES, V_L

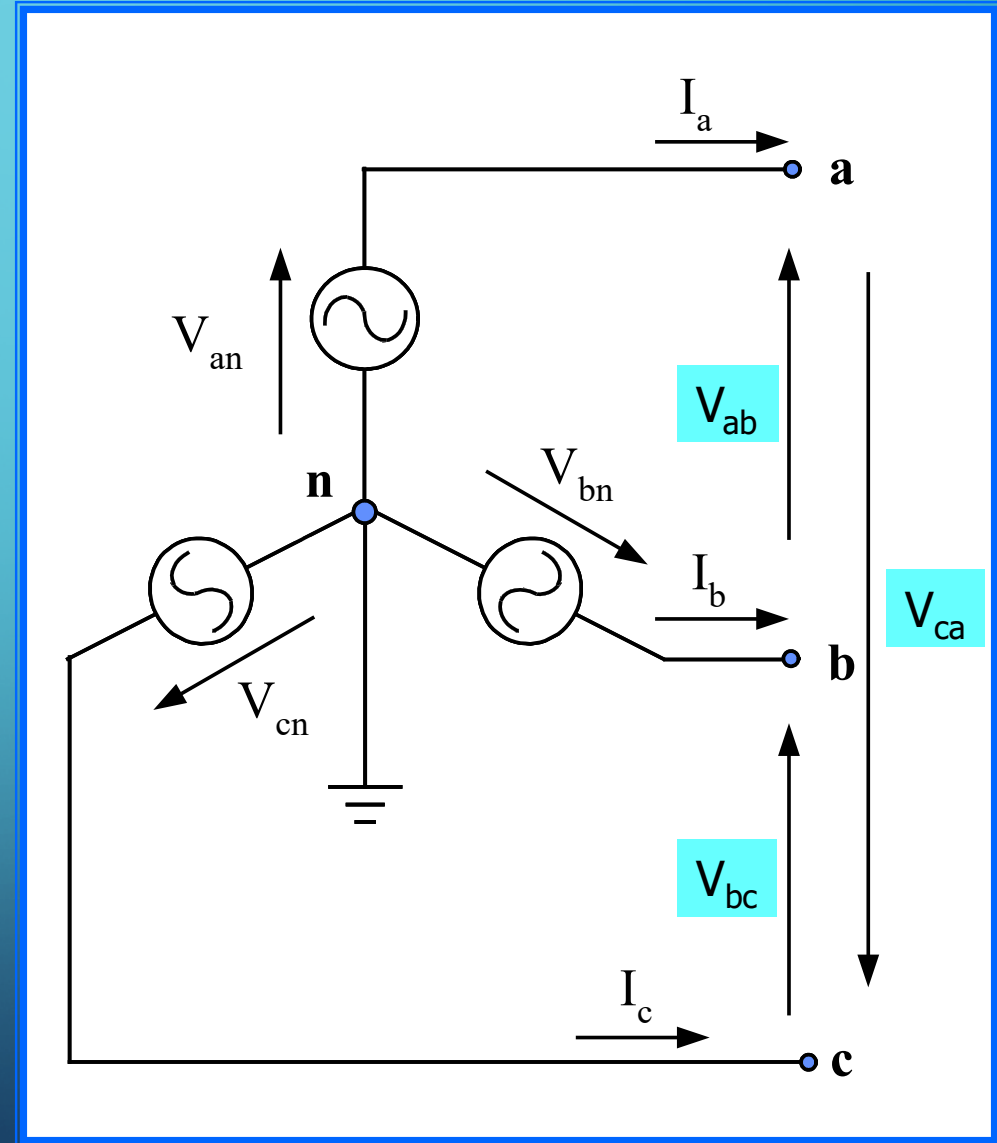- Line voltage is measured between any two of the three lines: line to line voltage.




LINE VOLTAGES, V_L

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

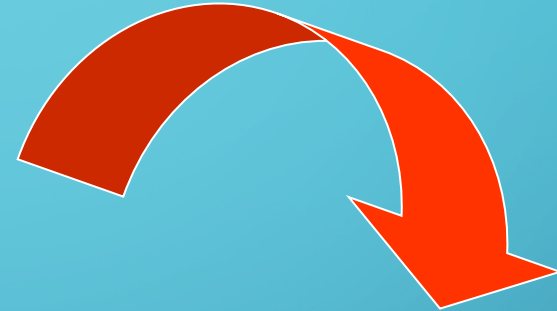

$$V_{ab} = \sqrt{3}V_M \angle 30^\circ$$

$$V_{bc} = \sqrt{3}V_M \angle -90^\circ$$

$$V_{ca} = \sqrt{3}V_M \angle 150^\circ$$

$$V_{an} = V_M \angle 0^\circ \quad \text{volt}$$

$$V_{bn} = V_M \angle -120^\circ \quad \text{volt}$$

$$V_{cn} = V_M \angle 120^\circ \quad \text{volt}$$

**PHASE
VOLTAGE (V_ϕ)**


**LINE
VOLTAGE
(V_L)**

$$V_{ab} = \sqrt{3} V_M \angle 30^\circ \quad \text{volt}$$

$$V_{bc} = \sqrt{3} V_M \angle -90^\circ \quad \text{volt}$$

$$V_{ca} = \sqrt{3} V_M \angle 150^\circ \quad \text{volt}$$

PHASE DIAGRAM OF V_L AND V_ϕ

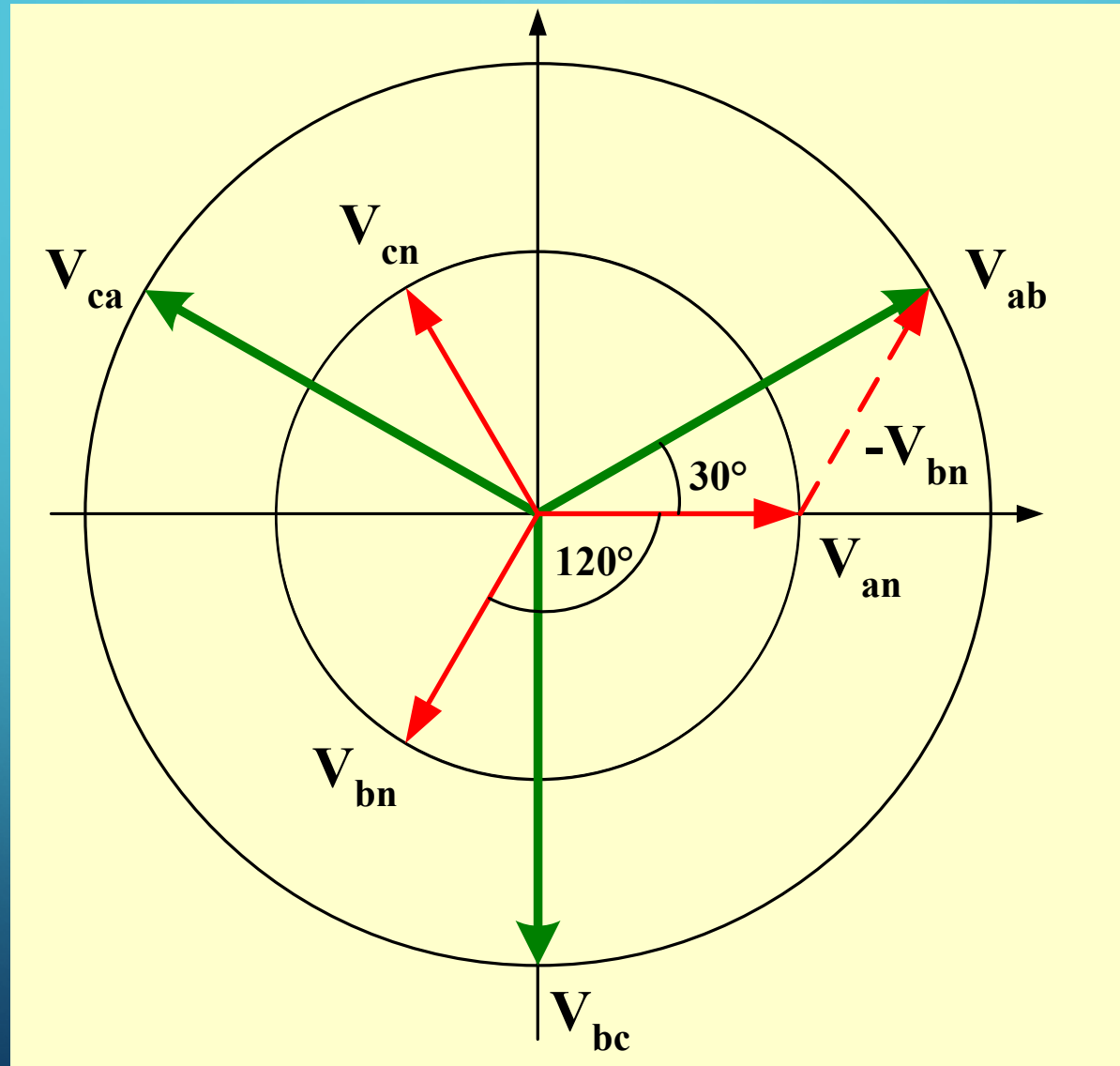

PROPERTIES OF PHASE VOLTAGE

- All phase voltages have the same magnitude,

$$V_{\phi} = |V_{an}| = |V_{bn}| = |V_{cn}|$$

- Out of phase

PROPERTIES OF LINE VOLTAGE

- All line voltages have the same magnitude,

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$

- Out of phase with each other by 120°

RELATIONSHIP BETWEEN V_ϕ AND V_L

1. Magnitude

$$|V_L| = \sqrt{3} |V_\phi|$$


2. Phase

- V_L **LEAD** their corresponding V_ϕ by **30°**

$$\angle V_L = \angle V_\phi + 30^\circ$$

EXAMPLE 1

- Calculate the line currents

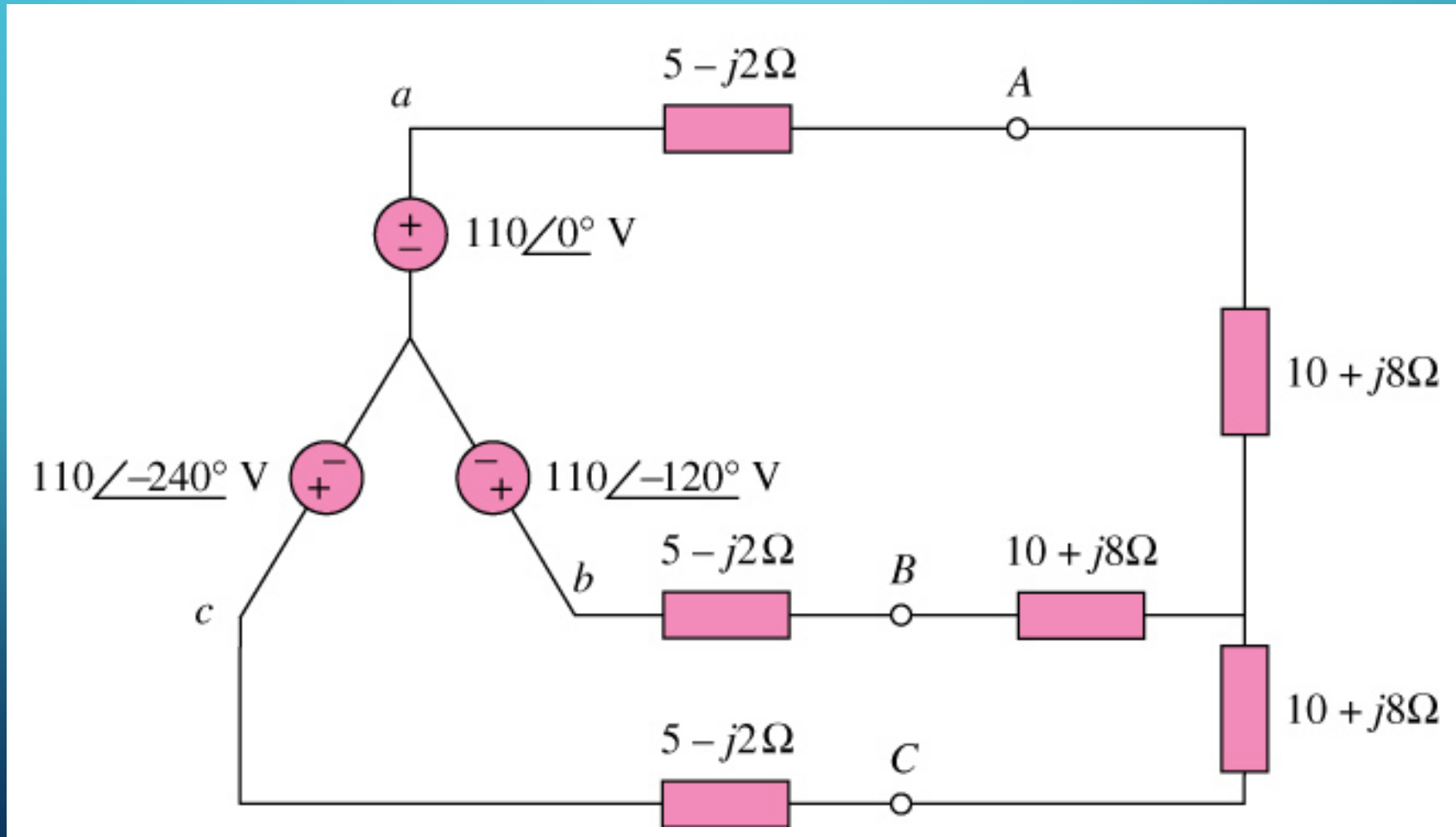

The image features a blue gradient background with white circuit-like lines in the corners. The lines consist of straight segments and small circles, resembling a printed circuit board layout. The text is centered in the middle of the image.

THANK FOR YOUR ATTENTION!