

VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of General Engineering Sciences and Labour Safety




TRANSIENTS IN ELECTRICAL CIRCUITS

by Associate Professor V. Hraniak



Introduction

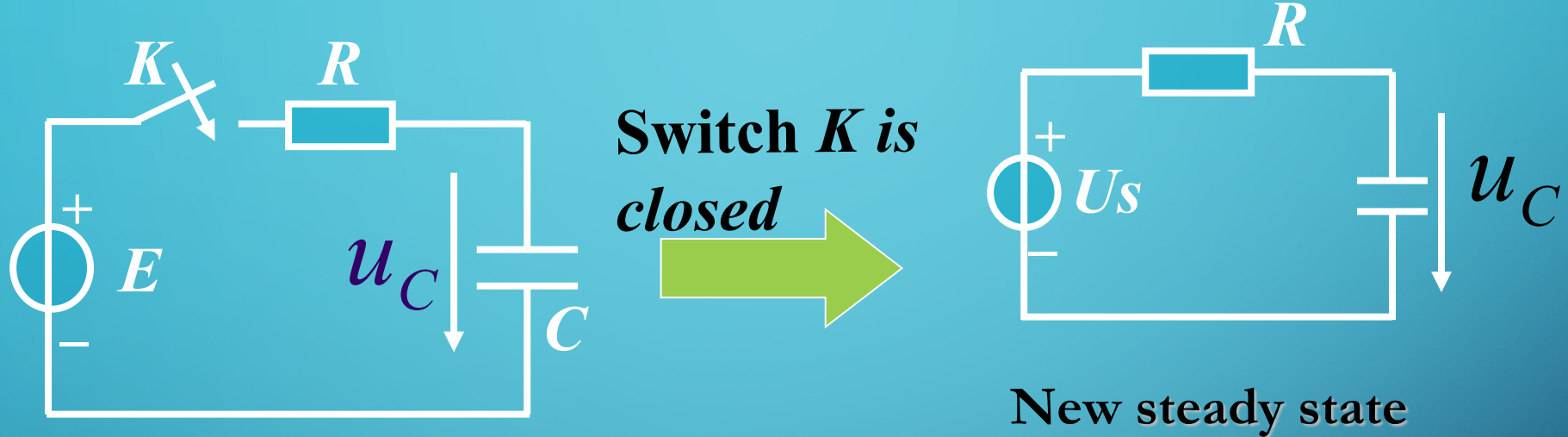
Conception of steady state and transient state



Old steady state


When $t=0$, $u_C(0)=0$

When $t=\infty$, $u_C(\infty)=U_s$

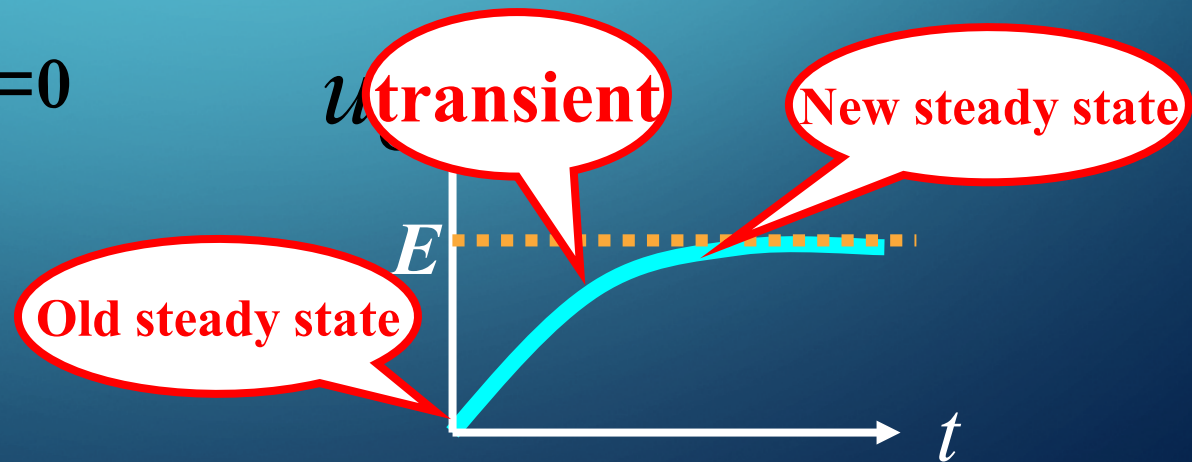

Why the transient response happens?

Resistance circuit


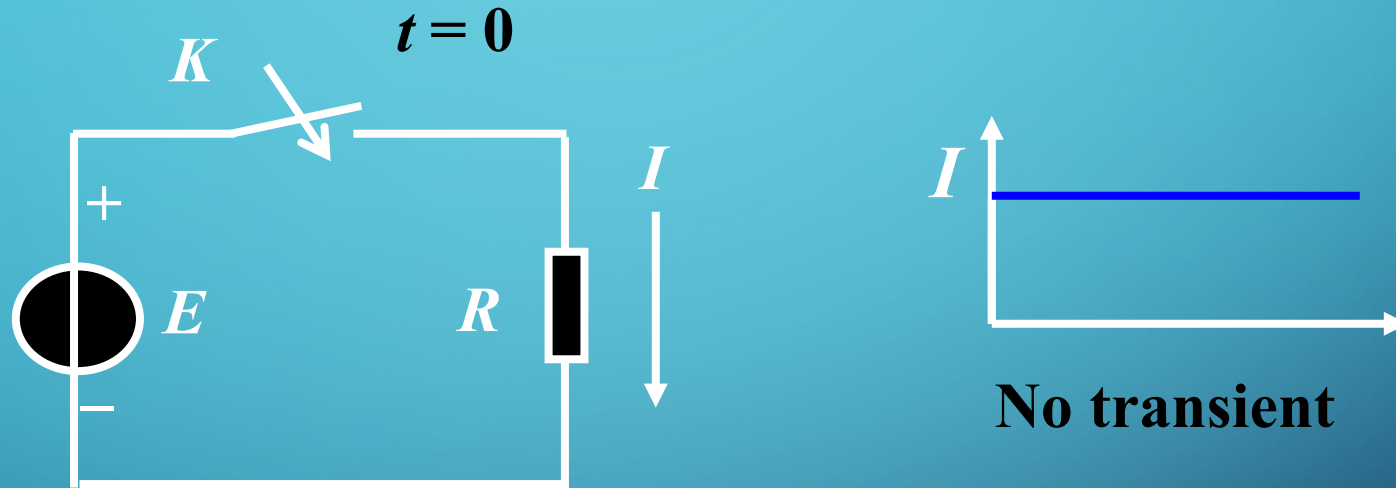


Resistor is a energy-consumption element, current is proportional to voltage, no transient response will happen even if changing source

Energy can not change instantly because of accumulating or decaying period.

Electric field energy ($W_C = \frac{1}{2} C u_C^2$)

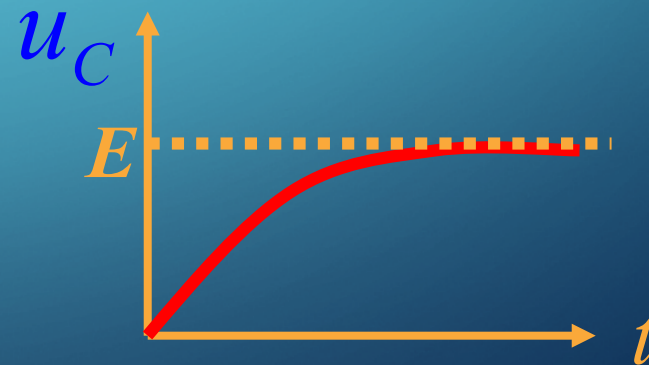
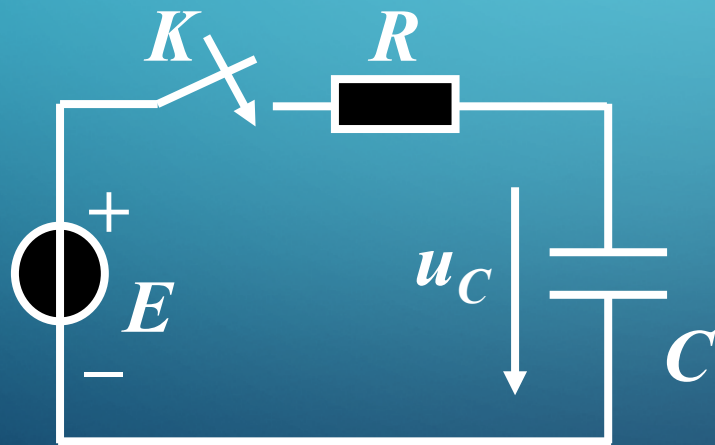
W_C Charging or discharging \longrightarrow u_C Change gradually



Energy can not change instantly because of accumulating or decaying period.

Magnetic field energy $(W_L = \frac{1}{2}Li_L^2)$

$W_L \rightarrow i_L$ Change gradually

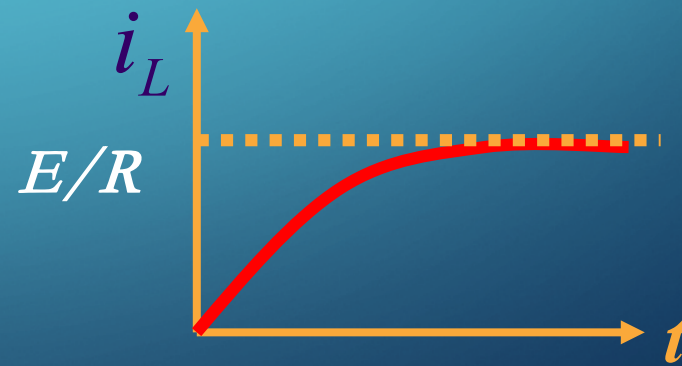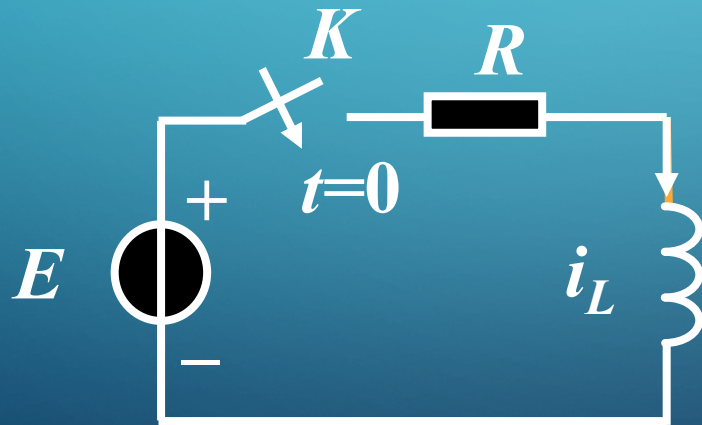

Transients

The time-varying currents and voltages resulting from the sudden application of sources, usually due to switching.

By writing circuit equations, we obtain integrodifferential equations.

The causes of transients:


1. Energy storage elements

-inductors and capacitors

u_C, i_L change gradually;

2. Changing circuit, such as switching source.

INITIAL STATE AND STEADY STATE

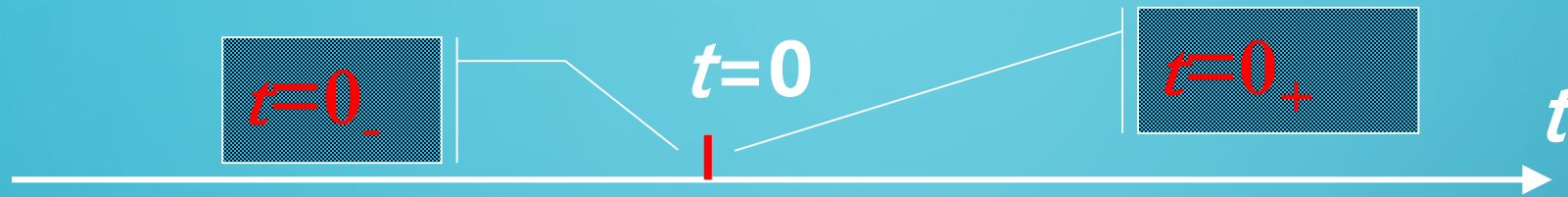

Assume changing circuit when $t=0$, then $t=0-$ is end point of old steady state; $t=0+$ is the start point of transient state.

$$\begin{cases} W_L(0_-) = W_L(0_+) \\ W_C(0_-) = W_C(0_+) \end{cases}$$

**The law of
changing circuit**

$$\begin{cases} i_L(0_-) = i_L(0_+) \\ u_C(0_-) = u_C(0_+) \end{cases}$$

From $t=0-$ to $t=0+$, i_L 、 u_C
change continuously.

DC STEADY STATE RESPONSE

The steps in determining the forced response or steady state response for *RLC* circuits with DC sources are:

1. Replace capacitances with open circuits.
2. Replace inductances with short circuits.
3. Solve the remaining circuit.

Example Find steady-state values of v_x and i_x in this circuit for $t \gg 0$.


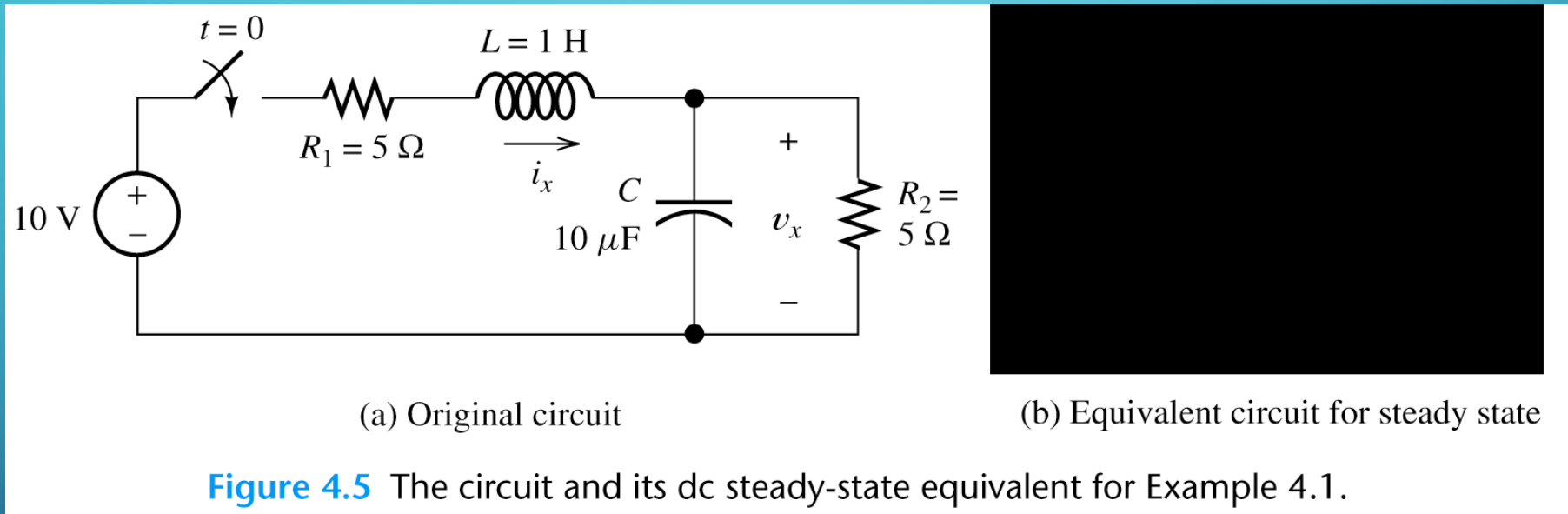



Figure 4.5 The circuit and its dc steady-state equivalent for Example 4.1.

Answer: $v_x = 5\text{V}$, $i_x = 1\text{A}$ $t \gg 0$

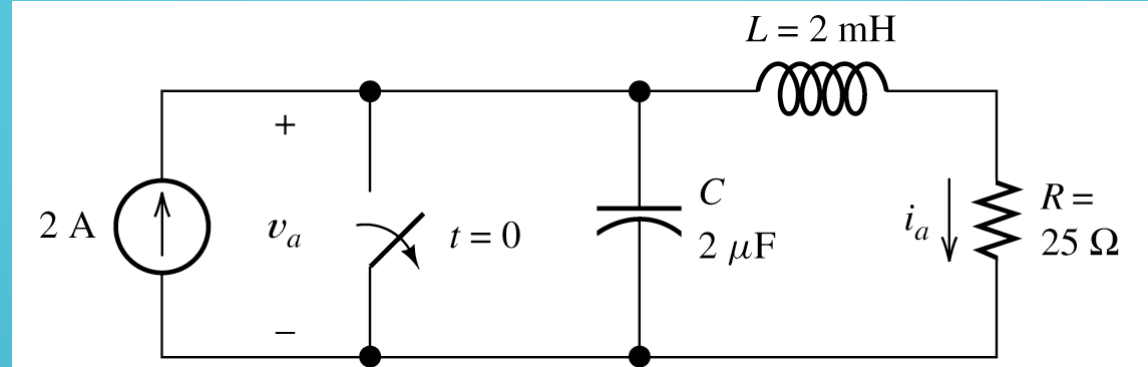Exercise 4.3 Find steady-state values of labeled currents and voltages for $t \gg 0$.



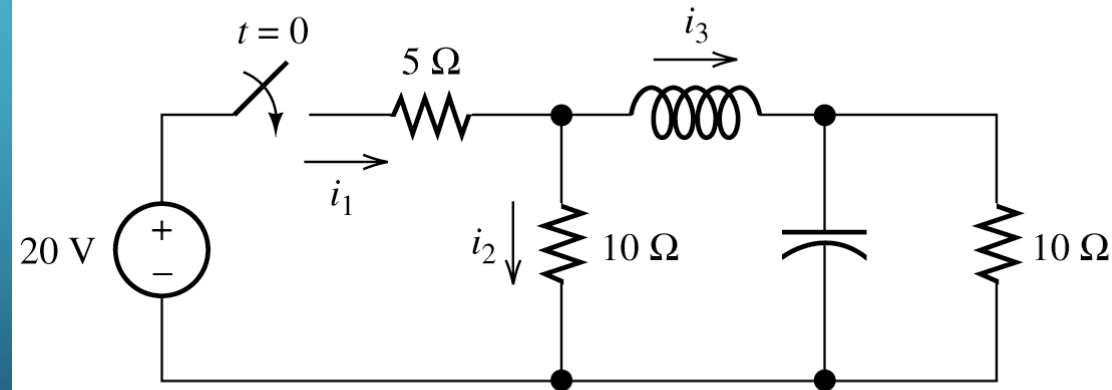Answer: $v_a = 50 \text{ V}$, $i_a = 2 \text{ A}$



(b)

$i_1 = 2 \text{ A}$, $i_2 = 1 \text{ A}$, $i_3 = 1 \text{ A}$

Figure 4.6 Circuits for Exercise 4.3.



HOW TO GET INITIAL VALUE

Exercise 1: Assuming old circuit is in DC steady state before switch K is closed. How to get $u_C(0+), i_R(0+)$?


Solution:

When $t=0-$, capacitor is considered as open circuit, we get equivalent circuit.
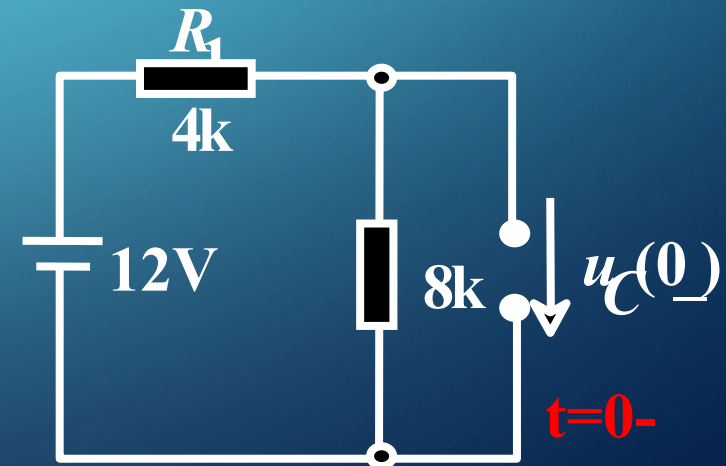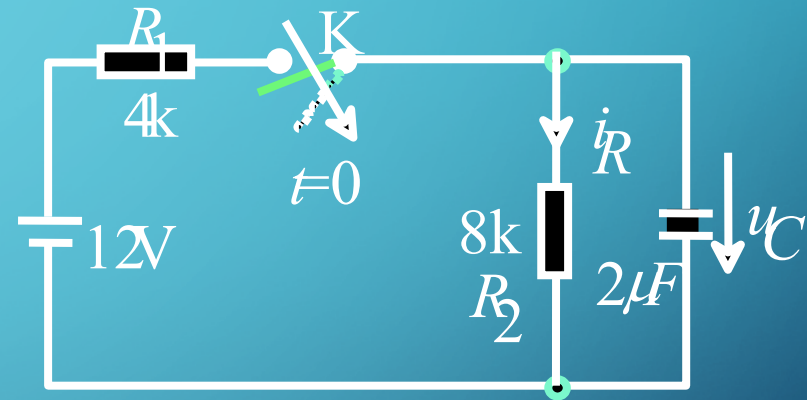
$$u_C(0_-) = \frac{8}{4+8} \times 12 = 8 \text{ V}$$




How to get initial value

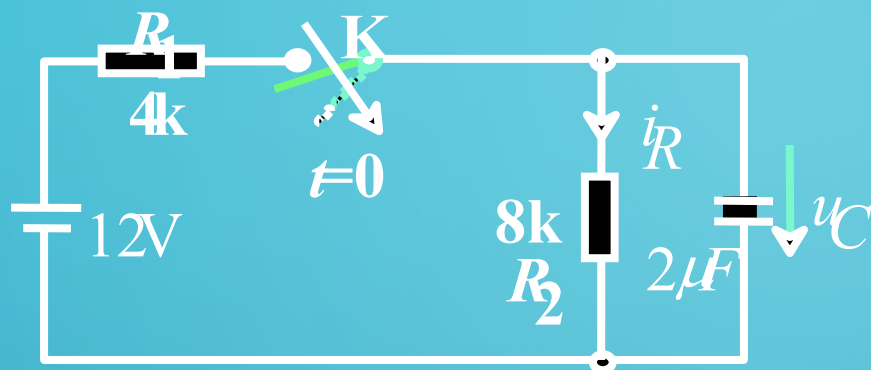


$$u_C(0_-) = \frac{8}{4+8} \times 12 = 8V$$

$$u_C(0_+) = u_C(0_-) = 8V$$

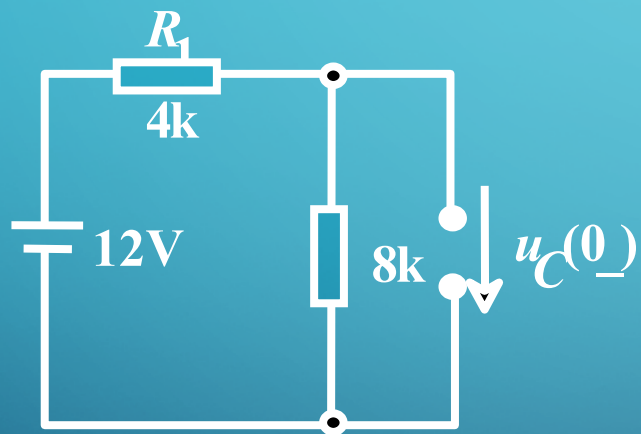substituting voltage source
for $u_C(0_+)$


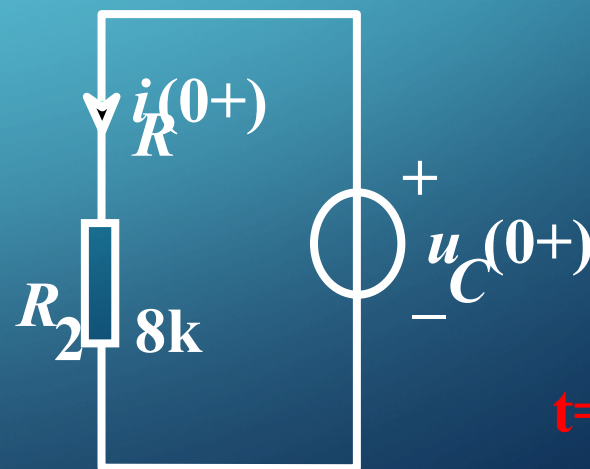
$$i_R(0_+) = \frac{u_C(0_+)}{R_2} = \frac{8}{8} = 1mA$$



$t=0_+$

How to get initial value

Exercise 2: Given by $R_1=4\Omega$, $R_2=6\Omega$, $R_3=3\Omega$, $C=0.1\mu\text{F}$, $L=1\text{mH}$, $U_S=36\text{V}$, switch S is closed for a long time.

Open the switch S when $t=0$, how to get the initial values of all elements?

