

VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of General Engineering Sciences and Labour Safety



TRANSIENTS IN THE SIMPLEST ELECTRICAL CIRCUITS

by Associate Professor V. Hraniak




FIRST-ORDER RC CIRCUITS

- **First-order circuit**

Only one (equivalent) capacitor or inductor is included in a linear circuit.




- **Equivalent circuit of First-order circuit**

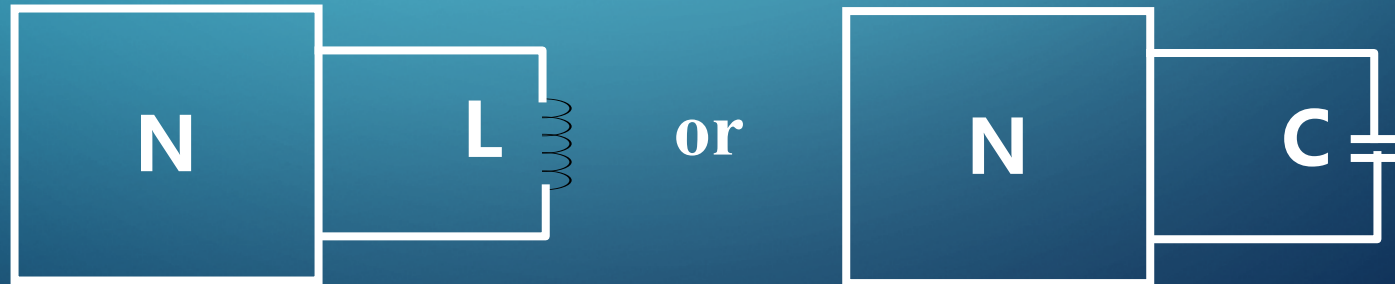Two parts: one (equivalent) capacitor or inductor; a two terminal network with resistance and sources.





First-order RC Circuits

- According to Thevenin Law

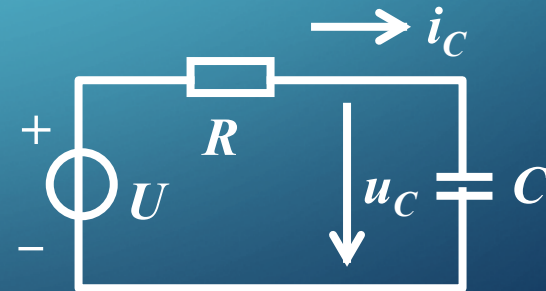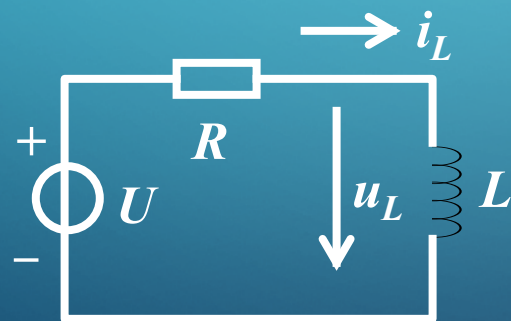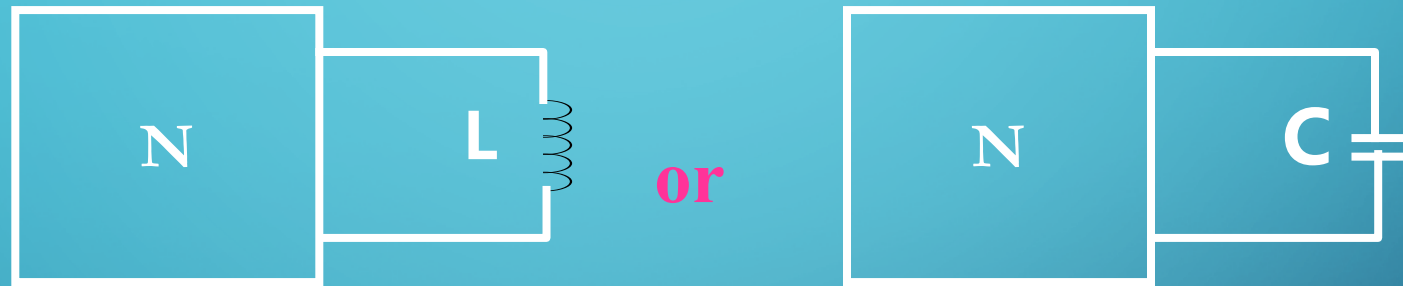

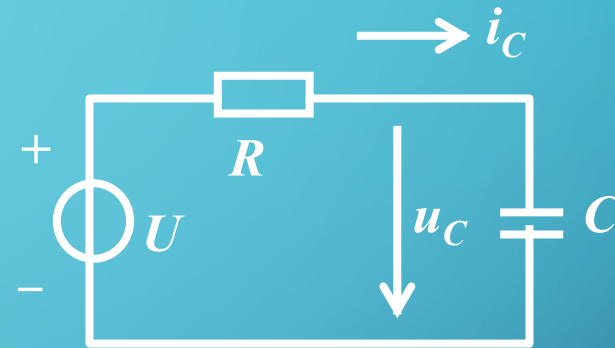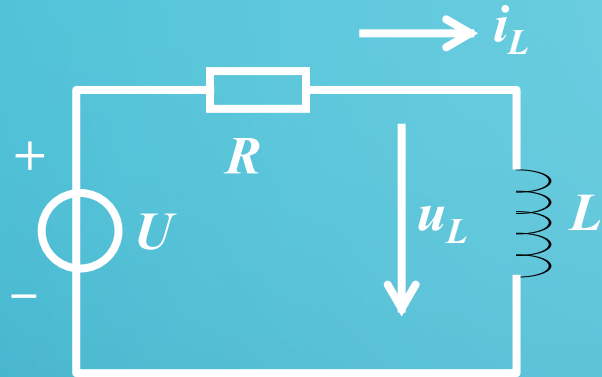Differential equation of first-order RC circuit




$$\begin{aligned}u_R + u_L &= U \\ Ri_L(t) + L \frac{di_L(t)}{dt} &= U \\ \frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) &= \frac{U}{R}\end{aligned}$$

$$\begin{aligned}u_R + u_C &= U \\ RC \frac{du_C}{dt} + u_C &= U\end{aligned}$$

FIRST-ORDER RC CIRCUITS

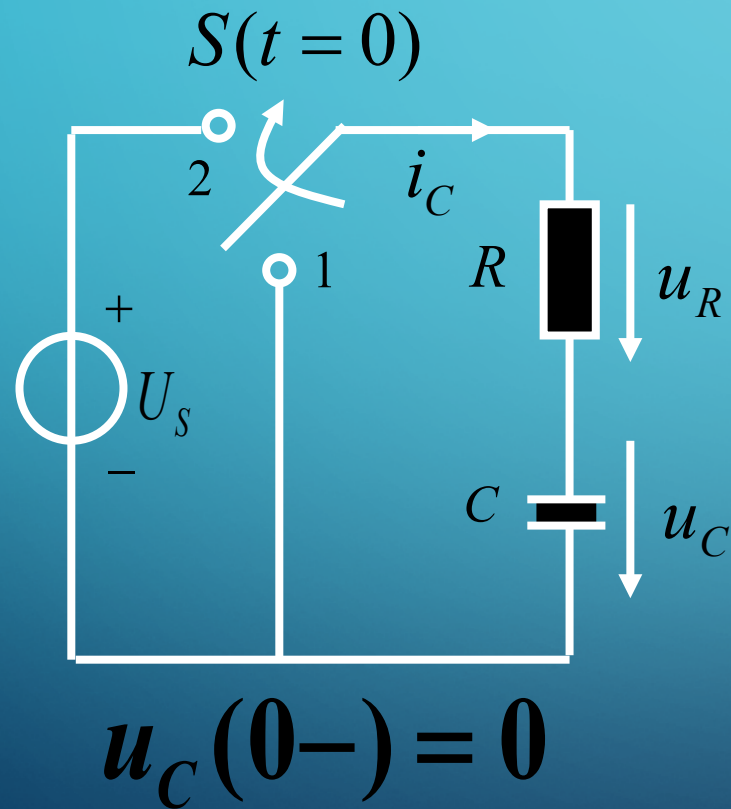
- **Example:** to find the transient response after changing circuit when $t=0$.



Solution:

$t \backslash f(t)$	u_C	u_R	i
$0-$	0	0	0
$0+$	0	U_S	$\frac{U_S}{R}$
∞	U_S	0	0

First-order RC Circuits

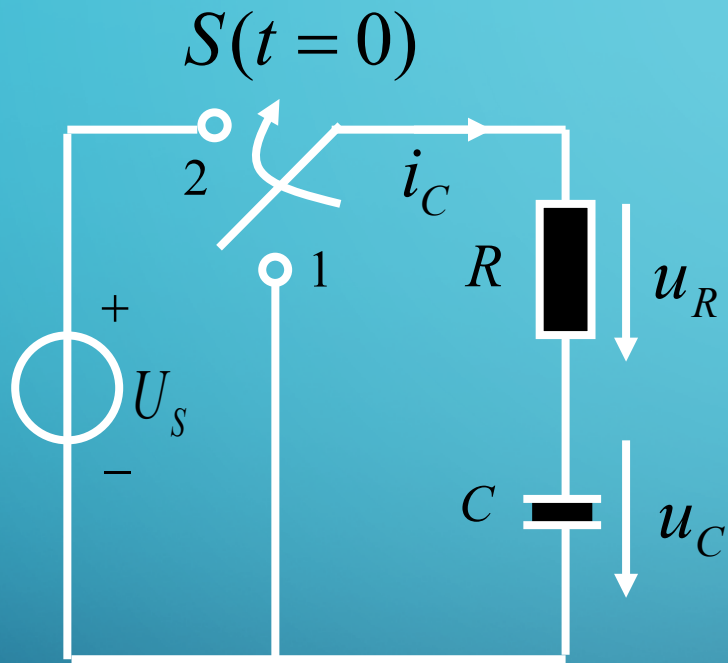

$$u_R + u_C = U_S$$


$$u_R = Ri \quad i = C \frac{du_C}{dt}$$

$$RC \frac{du_C}{dt} + u_C = U_S$$

$$u_C(0-) = 0$$

$$u_C(0+) = u_C(0-) = 0$$

First-order RC Circuits

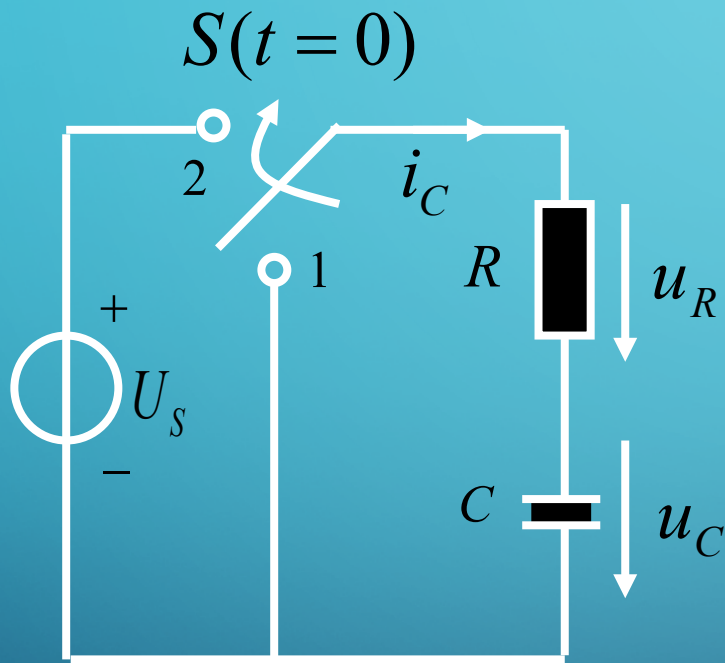

$$RC \frac{du_C}{dt} + u_C = U_S$$

$$u_C = u'_C + u''_C$$

$$u'_C = Ae^{st}$$


——homogeneous solution

$$u''_C$$

——particular solution

First-order RC Circuits

- homogeneous solution

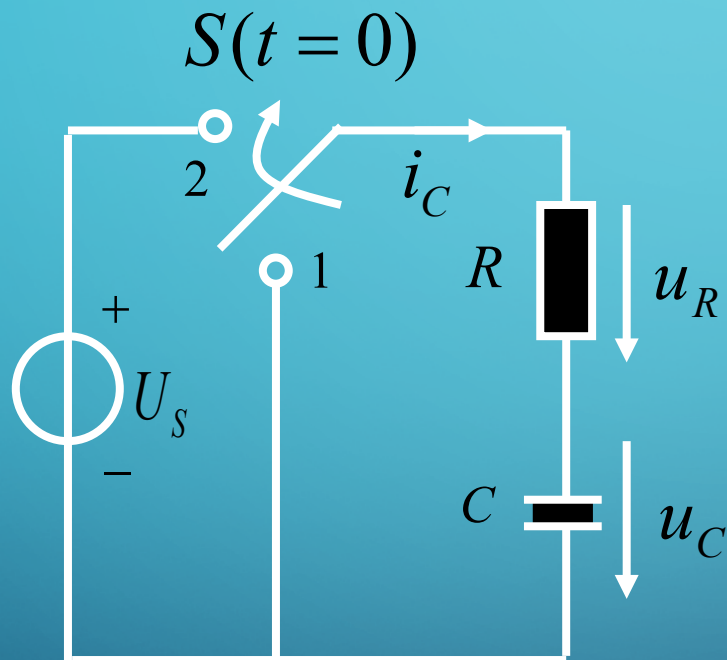

$$RC \frac{du_C}{dt} + u_C = U_S$$


$$RCs + 1 = 0$$

$$s = -\frac{1}{RC}$$

$$u'_C = Ae^{-\frac{1}{RC}t}$$

First-order RC Circuits

- Particular solution

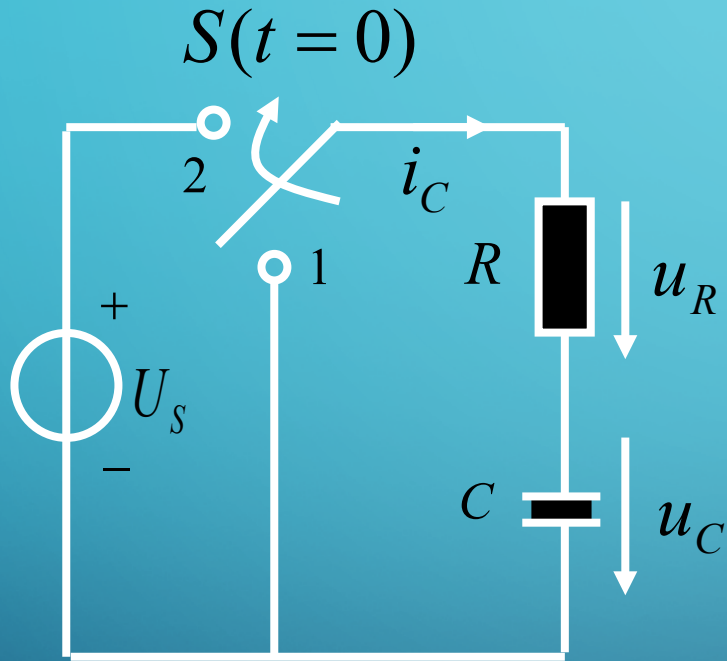

$$RC \frac{du_C}{dt} + u_C = U_S$$

Therefore

$$u_C'' = u_C(\infty) = U_S$$

Then, the final solution is

$$u_C = u_C' + u_C'' = Ae^{st} + U_S$$

First-order RC Circuits

- The solution of differential equation

$$u_C = u_C' + u_C'' = Ae^{st} + U_S$$

Substituting the initial condition:

$$u_C(0+) = u_C' + u_C'' = Ae^{s0} + U_S = 0$$

$$A = u_C(0+) - u_C(\infty) = -U_S$$

$$u_C(t) = u_C(\infty) + [u_C(0+) - u_C(\infty)]e^{-\frac{1}{RC}t}$$

$$= U_S - U_S e^{-\frac{1}{RC}t}$$

First-order RC Circuits

- The solution of differential equation

$$\tau = RC \quad \text{——Time constant}$$

$$u_C(t) = u_C(\infty) + [u_C(0+) - u_C(\infty)]e^{-\frac{t}{\tau}}$$

$$u_C(\infty) \quad \text{——Steady state value}$$

$$u_C(0+) \quad \text{——Initial value}$$

First-order RL Circuits


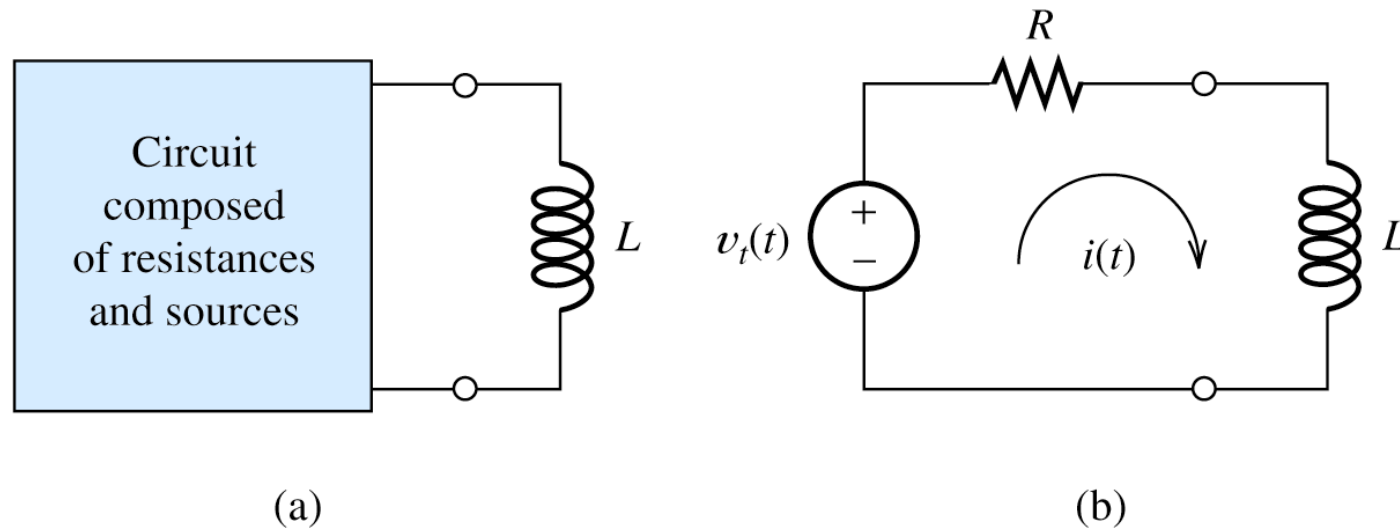


Figure 4.13 A circuit consisting of sources, resistances, and one inductance has an equivalent circuit consisting of a voltage source and a resistance in series with the inductance.


First-order RL Circuits

- Time constant

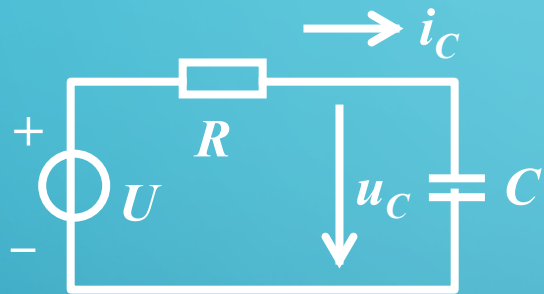

$$\tau = RC$$

$$RC \frac{du_C}{dt} + u_C = U$$

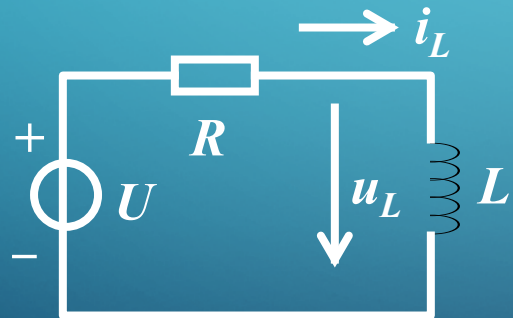

$$\frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) = \frac{U}{R}$$

$$\tau = L/R$$


- **Time constant reflects the length of transient period.**

t	τ	2τ	3τ	4τ	5τ	6τ	7τ
$e^{-t/\tau}$	36.8%	13.5%	5%	1.8%	0.3%	0.25%	0.09%

- **After one time constants, the transient response is equal to 36.8 percent of its initial value.**
- **After about five time constants, the transient response is over.**

- Time constant reflects the length of transient period.

- The curves versus time

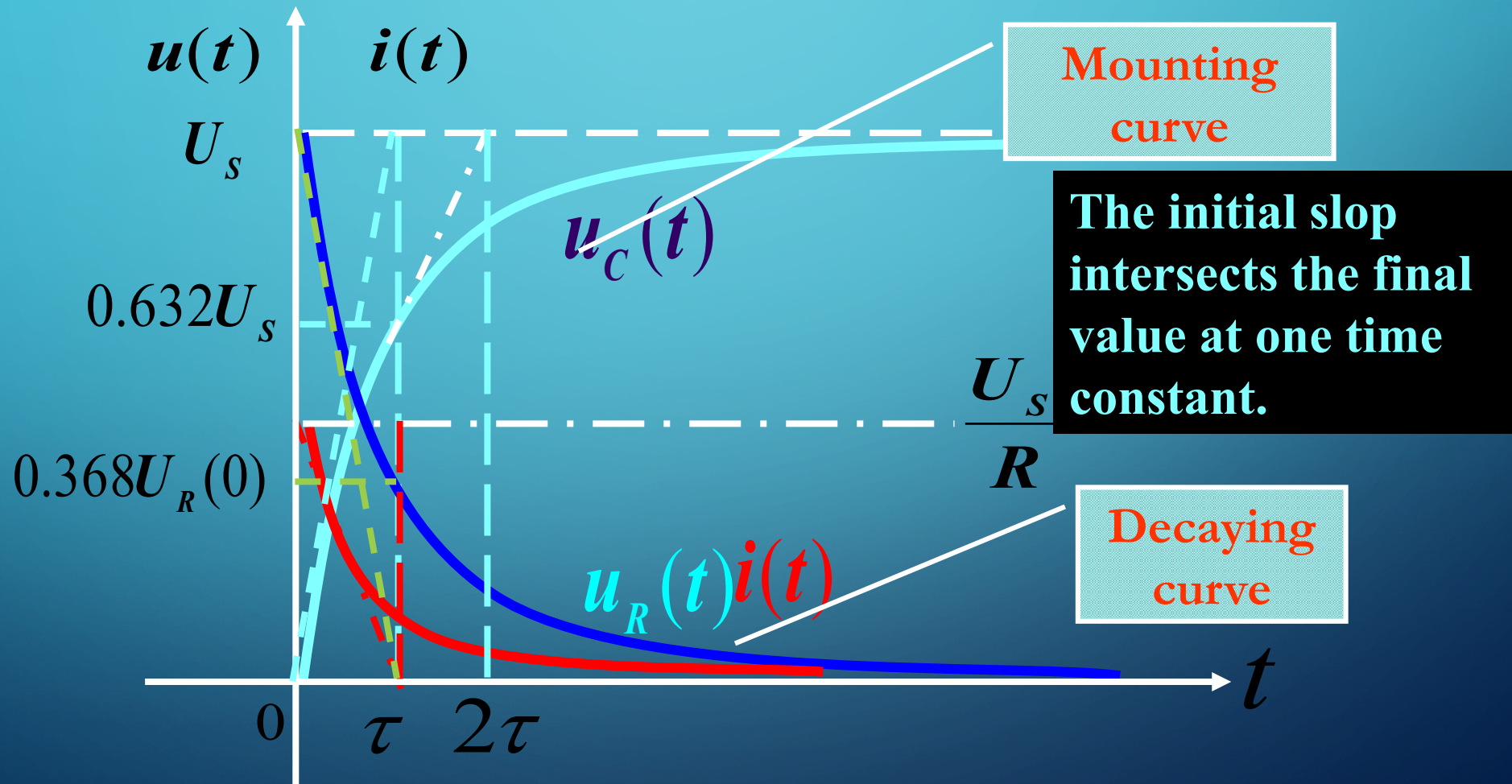

• **Example 4.2** Find voltage of $v(t)$ and current $i(t)$ in this circuit for $t > 0$.

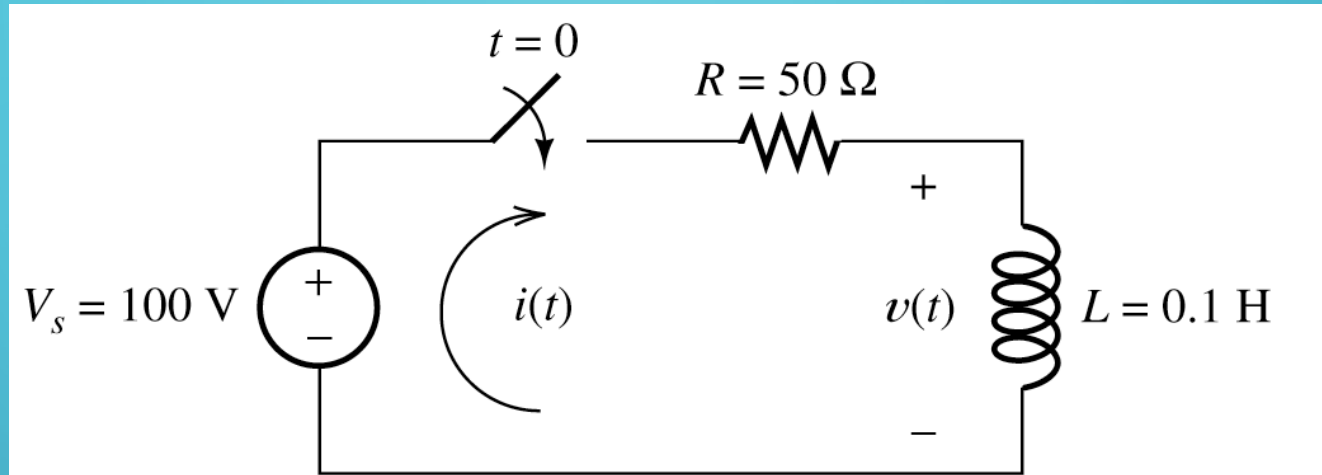


Figure 4.7 The circuit analyzed in Example 4.2.

Answer:

$$i(t) = 2 - 2e^{-\frac{t}{\tau}} \text{ (A)}, v(t) = 100e^{-\frac{t}{\tau}} \text{ (V)}$$

$$\tau = \frac{L}{R} = \frac{0.1}{50} = 2 \text{ (ms)}$$

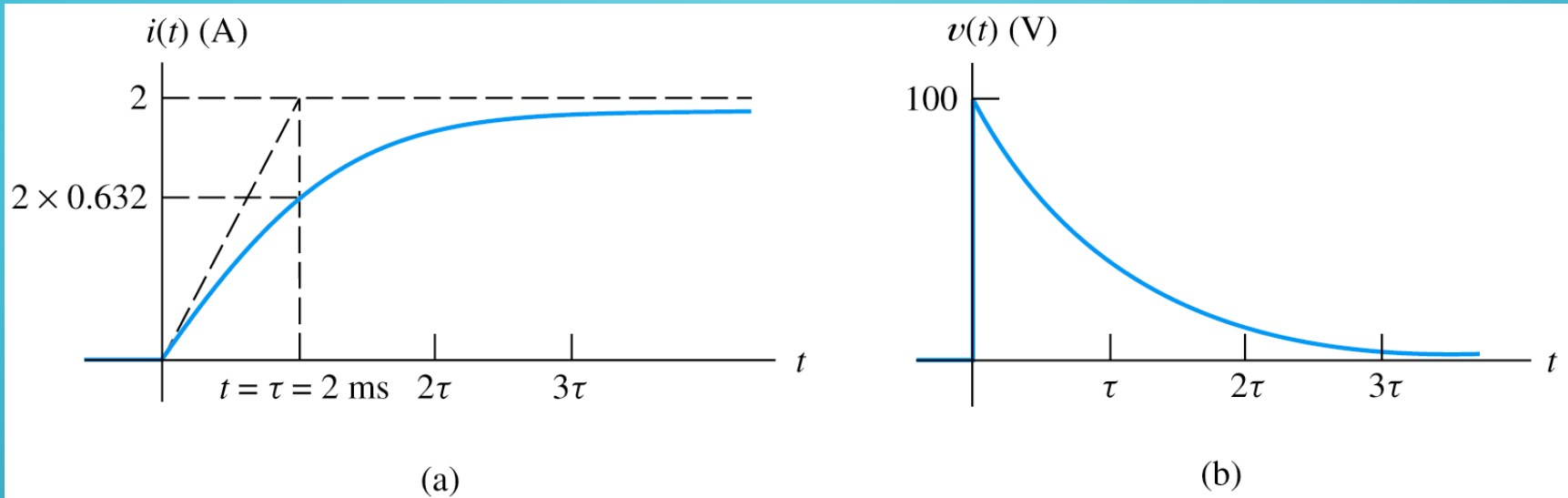


Figure 4.8 Current and voltage versus time for the circuit of Figure 4.7.

$$i(t) = 2 - 2e^{-\frac{t}{\tau}} \text{ (A)}, v(t) = 100e^{-\frac{t}{\tau}} \text{ (V)}$$

$$\tau = \frac{L}{R} = \frac{0.1}{50} = 2 \text{ (ms)}$$