

# VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of General Engineering Sciences and Labour Safety



## TRANSIENTS IN THE SIMPLEST ELECTRICAL CIRCUITS

by Associate Professor V. Hraniak




# FIRST-ORDER RC CIRCUITS

- **First-order circuit**

Only one (equivalent) capacitor or inductor is included in a linear circuit.




- **Equivalent circuit of First-order circuit**

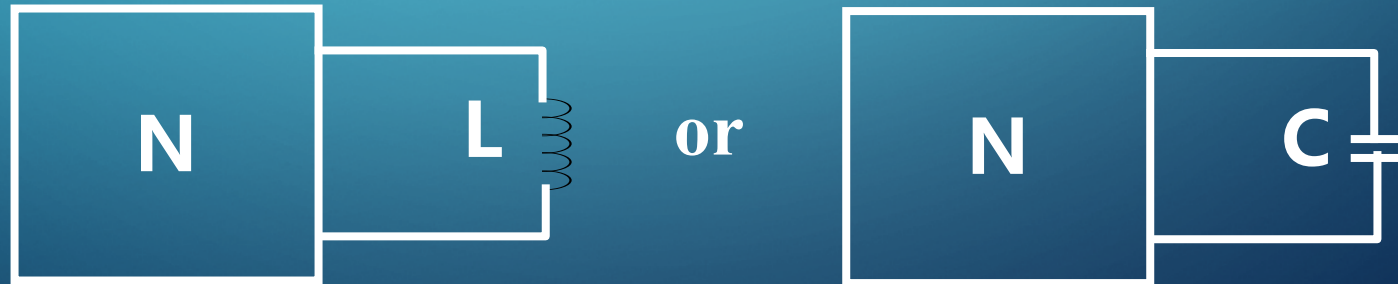Two parts: one (equivalent) capacitor or inductor; a two terminal network with resistance and sources.





# First-order RC Circuits

- According to Thevenin Law

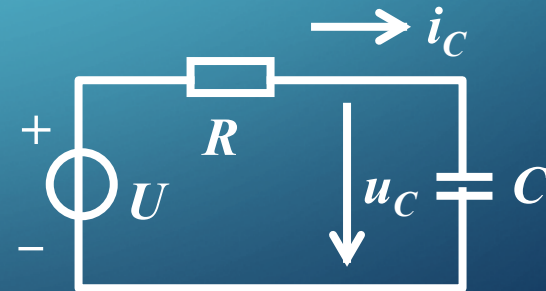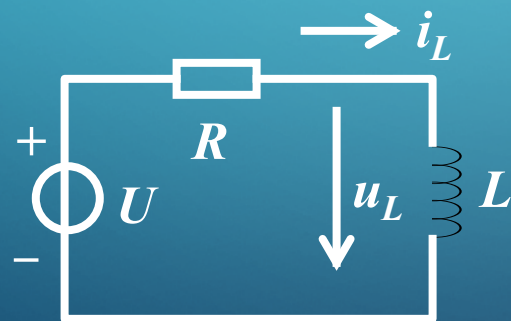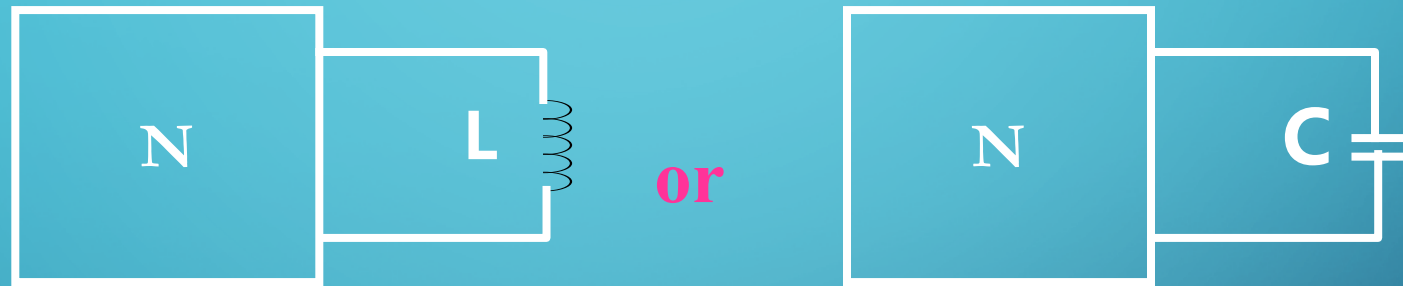
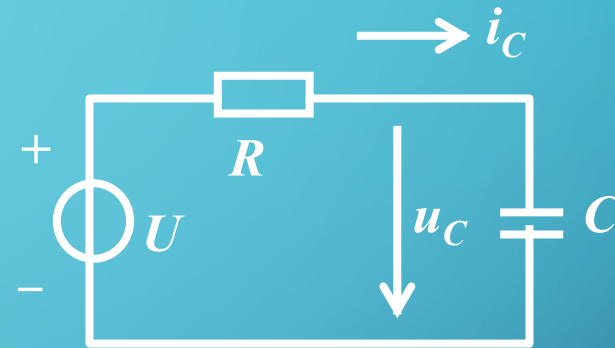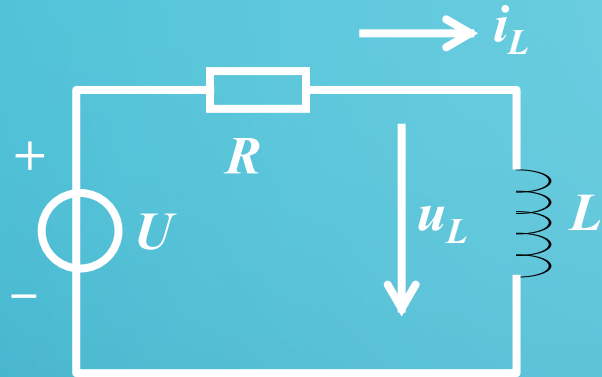
# Differential equation of first-order RC circuit




$$\begin{aligned}u_R + u_L &= U \\ Ri_L(t) + L \frac{di_L(t)}{dt} &= U \\ \frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) &= \frac{U}{R}\end{aligned}$$

$$\begin{aligned}u_R + u_C &= U \\ RC \frac{du_C}{dt} + u_C &= U\end{aligned}$$

# FIRST-ORDER RC CIRCUITS

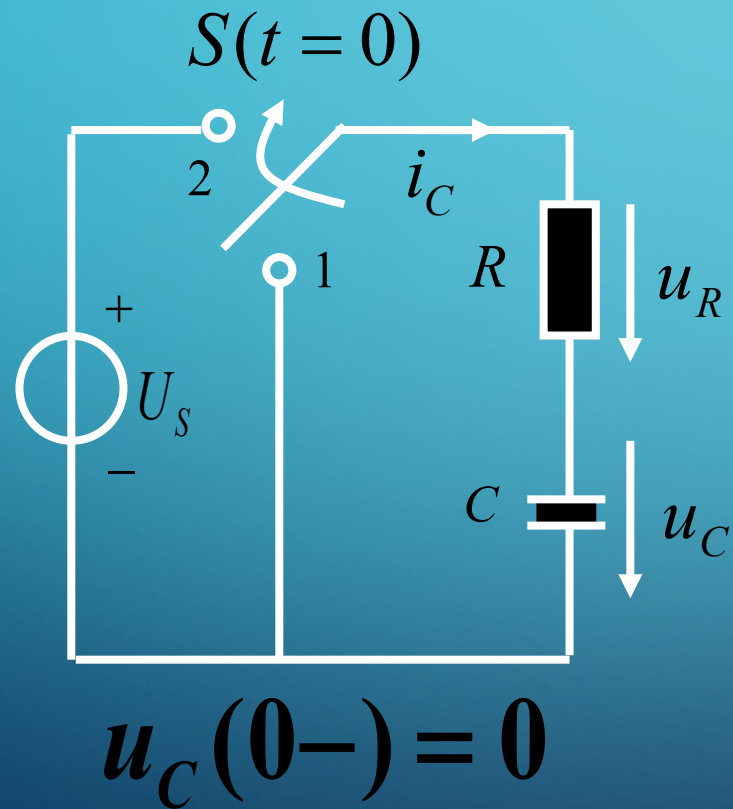
- Example: to find the transient response after changing circuit when  $t=0$ .



**Solution:**

$t \backslash f(t)$	$u_C$	$u_R$	$i$
$0-$	$0$	$0$	$0$
$0+$	$0$	$U_S$	$\frac{U_S}{R}$
$\infty$	$U_S$	$0$	$0$

# First-order RC Circuits

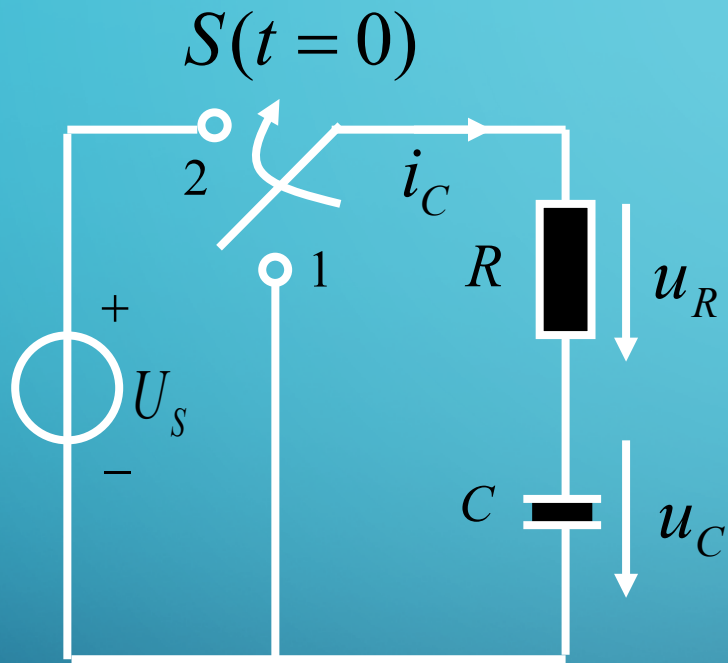

$$u_R + u_C = U_S$$


$$u_R = Ri \quad i = C \frac{du_C}{dt}$$

$$RC \frac{du_C}{dt} + u_C = U_S$$

$$u_C(0-) = 0$$

$$u_C(0+) = u_C(0-) = 0$$

# First-order RC Circuits

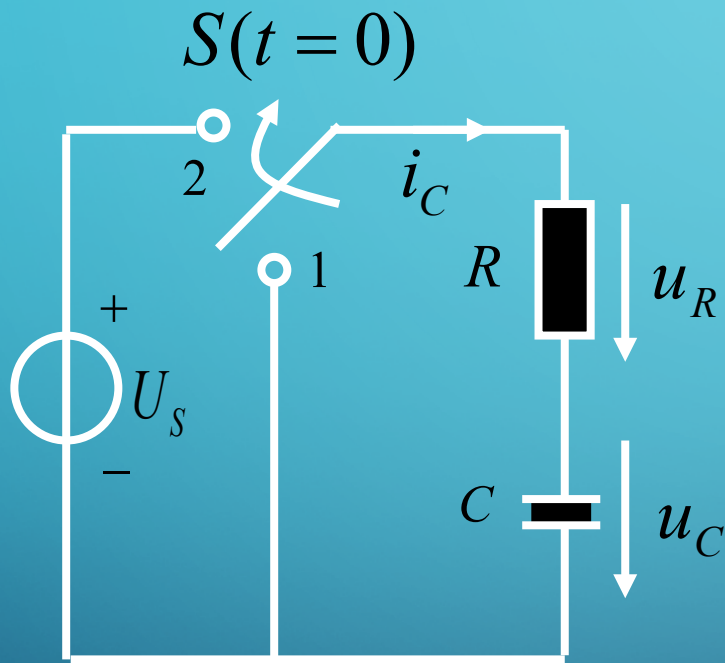

$$RC \frac{du_C}{dt} + u_C = U_S$$

$$u_C = u'_C + u''_C$$

$$u'_C = Ae^{st}$$


——homogeneous solution

$$u''_C$$

——particular solution

# First-order RC Circuits

- homogeneous solution

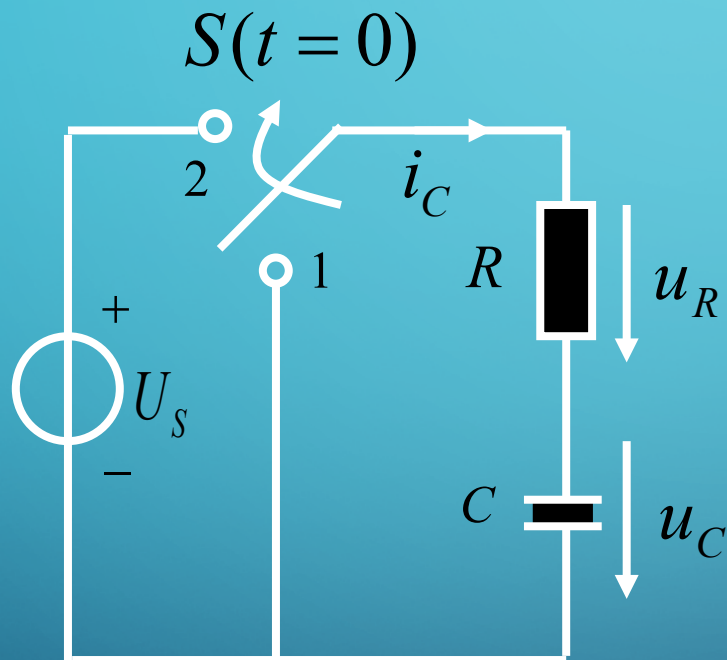

$$RC \frac{du_C}{dt} + u_C = U_S$$

$$RCs + 1 = 0$$


$$s = -\frac{1}{RC}$$

$$u'_C = Ae^{-\frac{1}{RC}t}$$



# First-order RC Circuits

- Particular solution

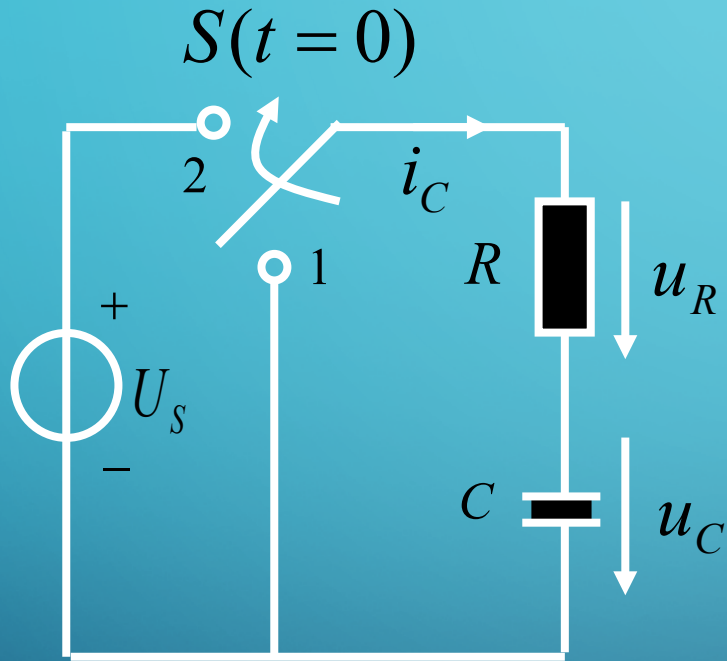

$$RC \frac{du_C}{dt} + u_C = U_S$$

Therefore

$$u_C'' = u_C(\infty) = U_S$$

Then, the final solution is

$$u_C = u_C' + u_C'' = Ae^{st} + U_S$$

# First-order RC Circuits

- The solution of differential equation

$$u_C = u_C' + u_C'' = Ae^{st} + U_S$$

Substituting the initial condition:

$$u_C(0+) = u_C' + u_C'' = Ae^{s0} + U_S = 0$$

$$A = u_C(0+) - u_C(\infty) = -U_S$$

$$u_C(t) = u_C(\infty) + [u_C(0+) - u_C(\infty)]e^{-\frac{1}{RC}t}$$

$$= U_S - U_S e^{-\frac{1}{RC}t}$$

# First-order RC Circuits

- The solution of differential equation


$$\tau = RC \quad \text{——Time constant}$$

$$u_C(t) = u_C(\infty) + [u_C(0+) - u_C(\infty)]e^{-\frac{t}{\tau}}$$

$$u_C(\infty) \quad \text{——Steady state value}$$

$$u_C(0+) \quad \text{——Initial value}$$


# First-order RL Circuits

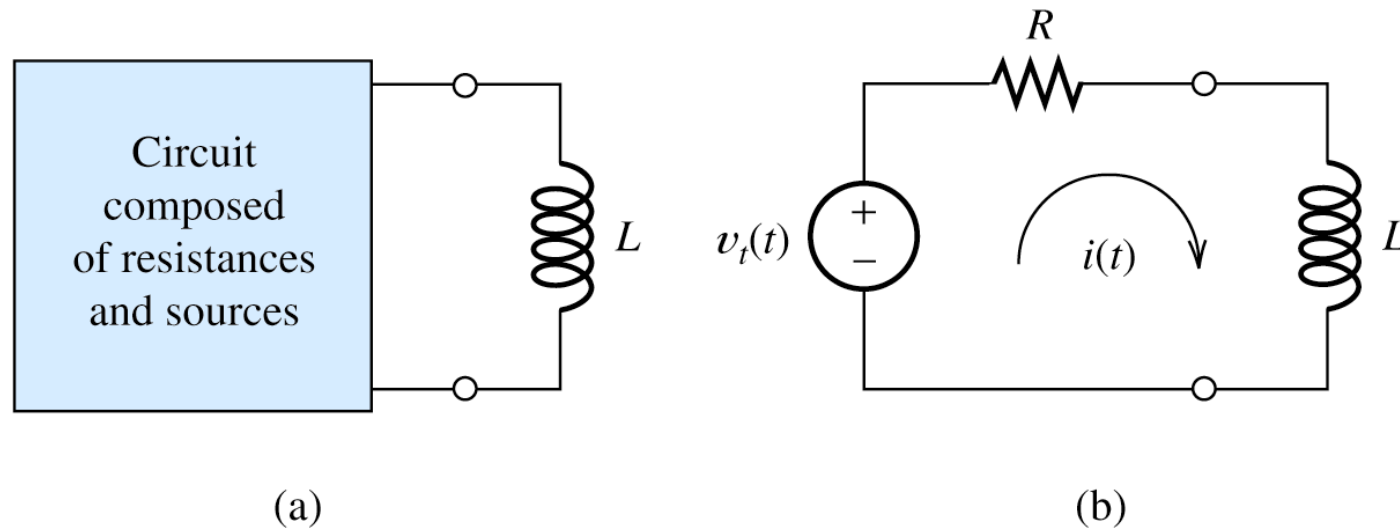

**Figure 4.13** A circuit consisting of sources, resistances, and one inductance has an equivalent circuit consisting of a voltage source and a resistance in series with the inductance.


# First-order RL Circuits

- Time constant

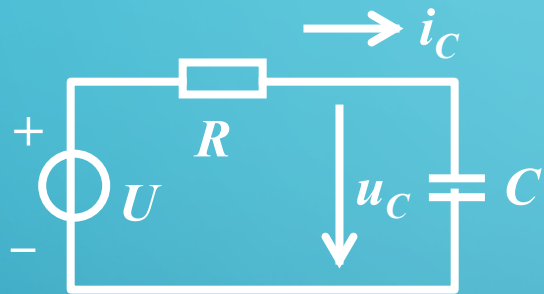

$$\tau = RC$$

$$RC \frac{du_C}{dt} + u_C = U$$

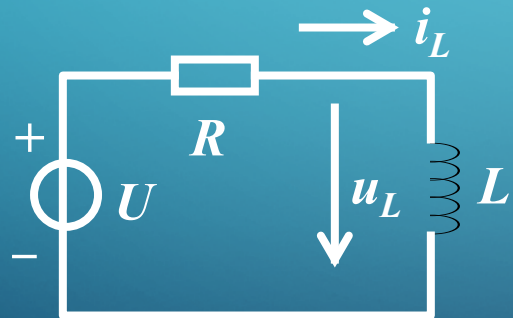

$$\frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) = \frac{U}{R}$$

$$\tau = L/R$$

- **Time constant reflects the length of transient period.**


$t$	$\tau$	$2\tau$	$3\tau$	$4\tau$	$5\tau$	$6\tau$	$7\tau$
$e^{-t/\tau}$	36.8%	13.5%	5%	1.8%	0.3%	0.25%	0.09%

- **After one time constants, the transient response is equal to 36.8 percent of its initial value.**


- **After about five time constants, the transient response is over.**

- Time constant reflects the length of transient period.

- The curves versus time

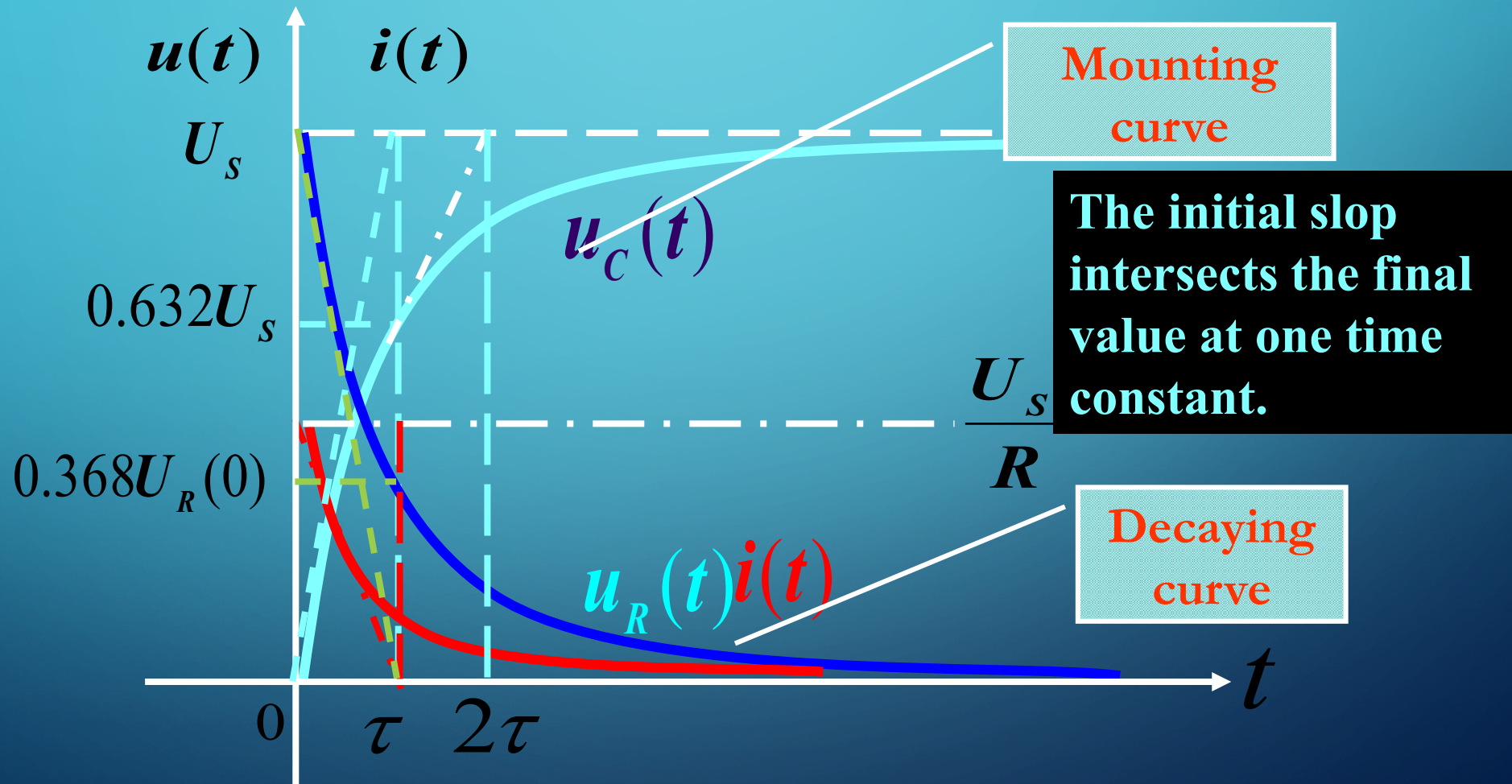

• **Example 4.2** Find voltage of  $v(t)$  and current  $i(t)$  in this circuit for  $t > 0$ .

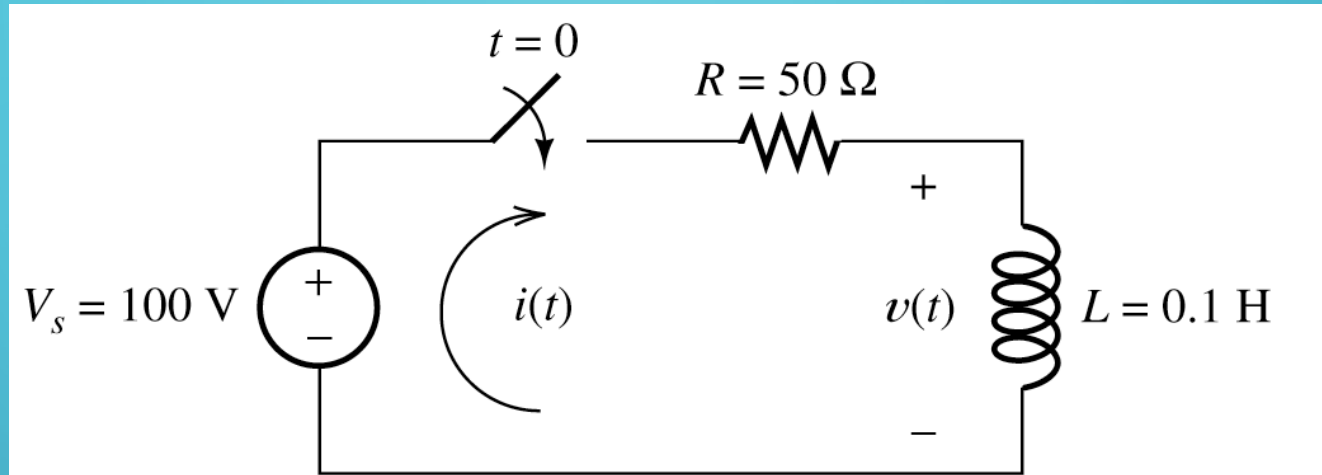


**Figure 4.7** The circuit analyzed in Example 4.2.

**Answer:**

$$i(t) = 2 - 2e^{-\frac{t}{\tau}} \text{ (A)}, v(t) = 100e^{-\frac{t}{\tau}} \text{ (V)}$$

$$\tau = \frac{L}{R} = \frac{0.1}{50} = 2 \text{ (ms)}$$



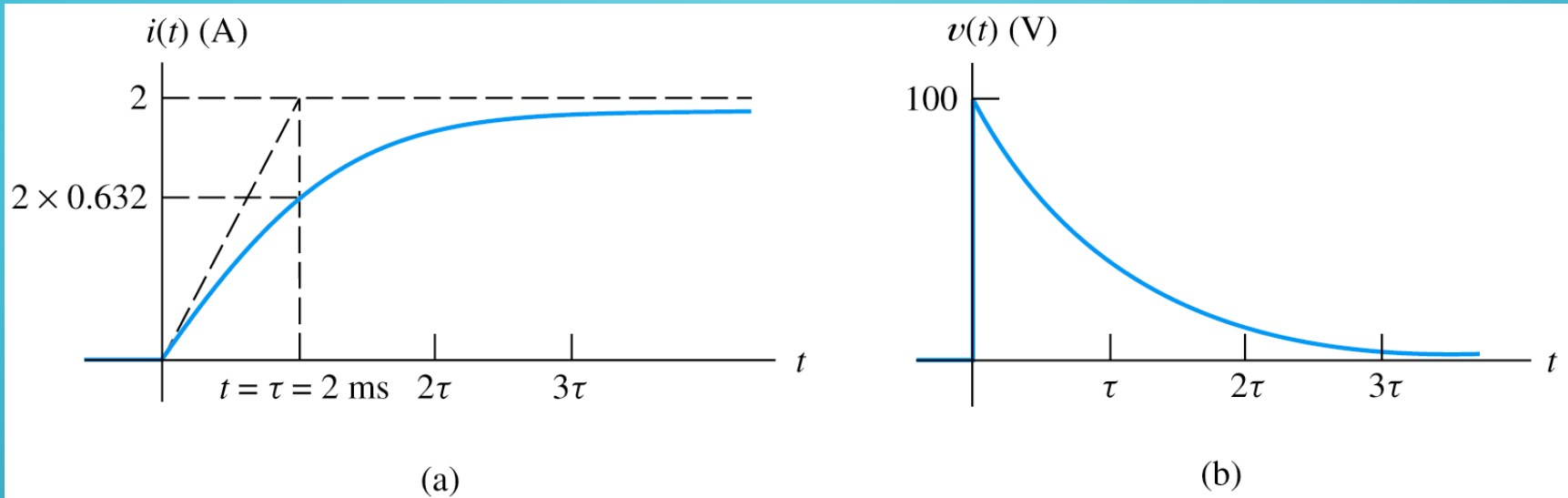

**Figure 4.8** Current and voltage versus time for the circuit of Figure 4.7.

$$i(t) = 2 - 2e^{-\frac{t}{\tau}} \text{ (A)}, v(t) = 100e^{-\frac{t}{\tau}} \text{ (V)}$$

$$\tau = \frac{L}{R} = \frac{0.1}{50} = 2 \text{ (ms)}$$